

Control Unit

Hamacher:

Chapter 7.1,7.2,7.4,7.5

Basic Components of Processor

- ALU
- Control Unit
- Registers
- Internal bus
- External bus
 - The registers, ALU, and interconnecting bus are collectively referred to as **datapath**

A Simple Processor Organization

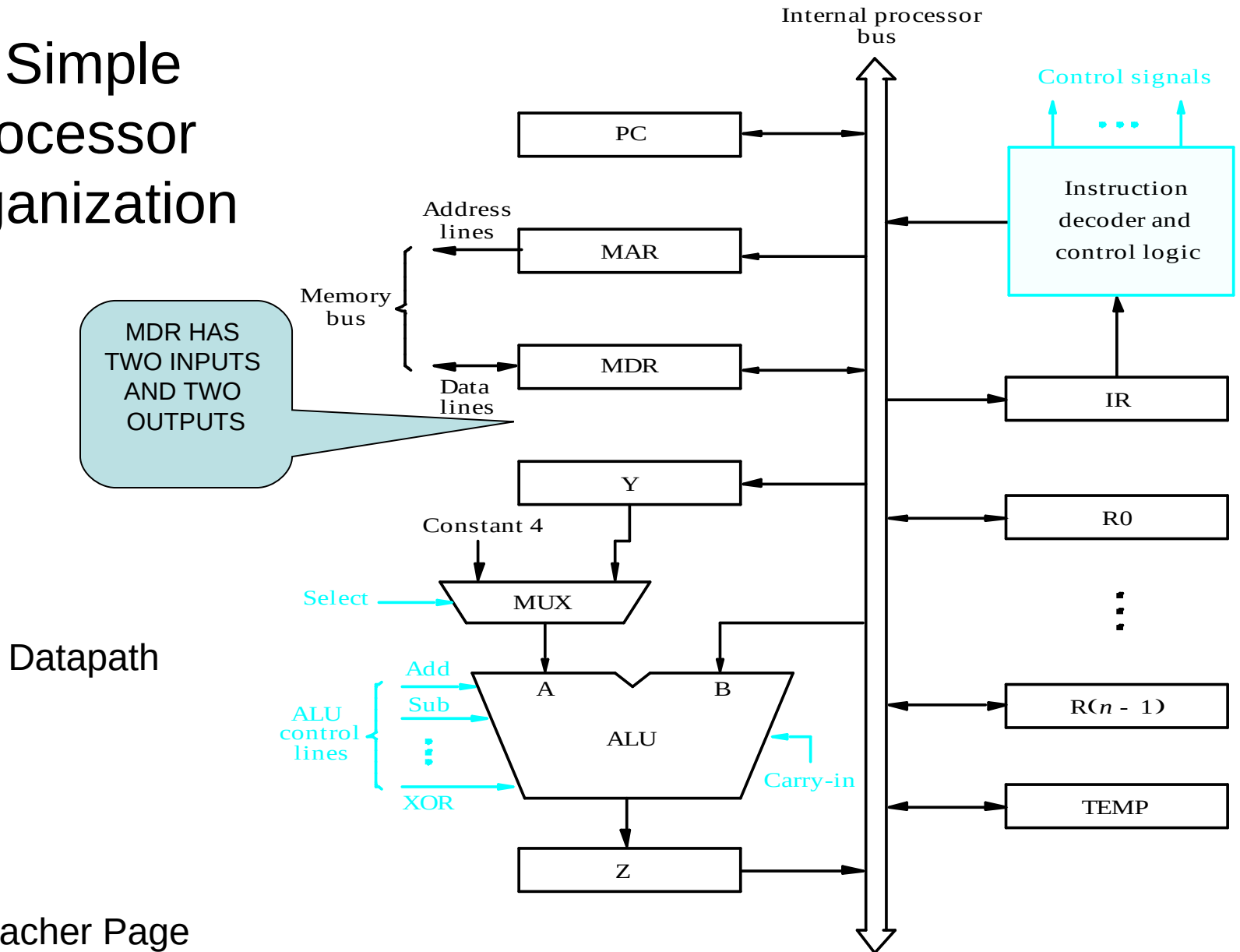


Figure 7.1. Single-bus organization of the datapath inside a processor.

Register Transfers

 


Figure 7.2. Input and output gating for the registers in Figure 7.1.

Register Transfers

- All operations and data transfers are controlled by the processor clock.

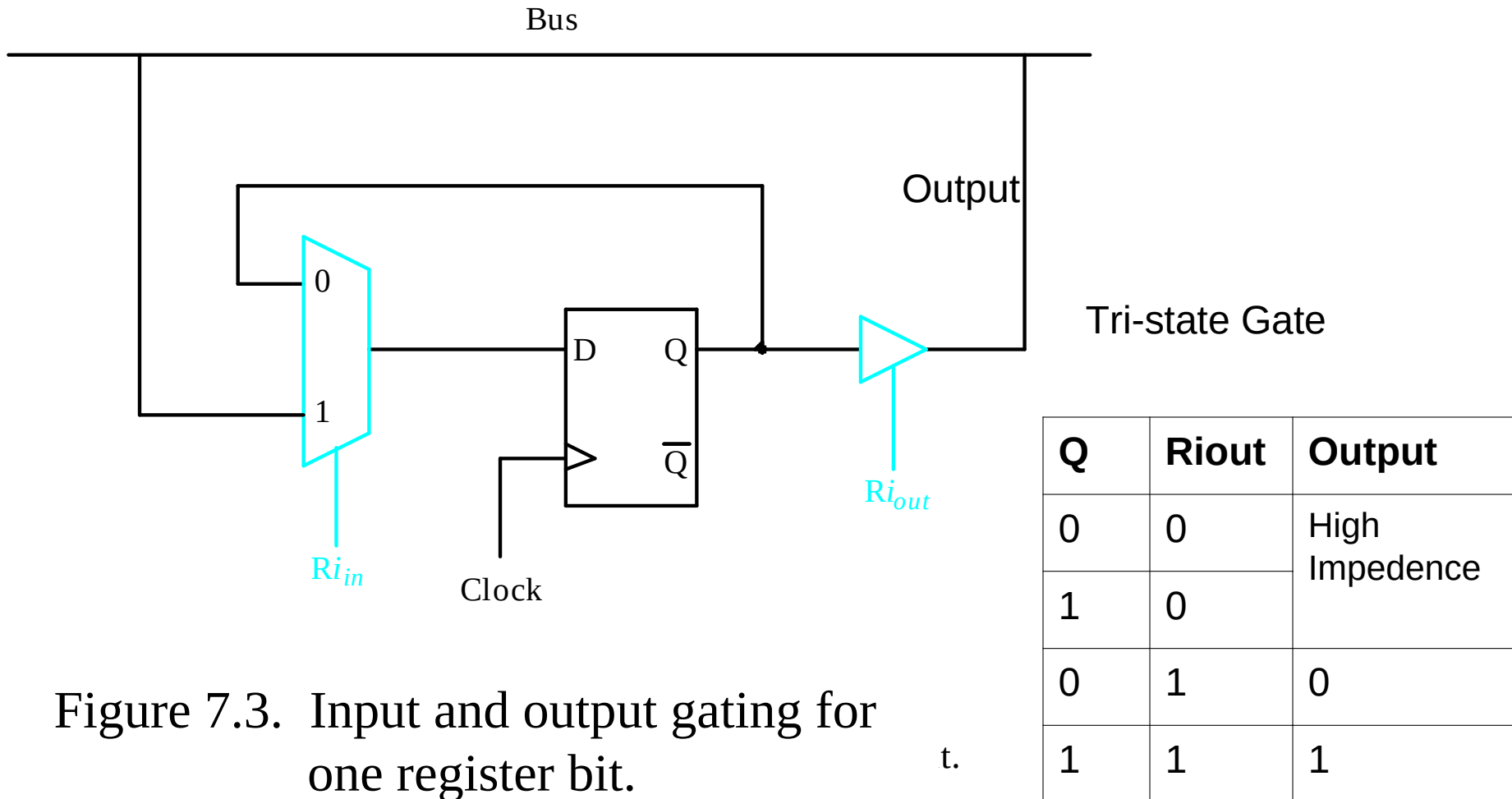


Figure 7.3. Input and output gating for one register bit.

Fetching a Word from Memory

• Address into MAR; issue Read operation; WMFC

• data into MDR

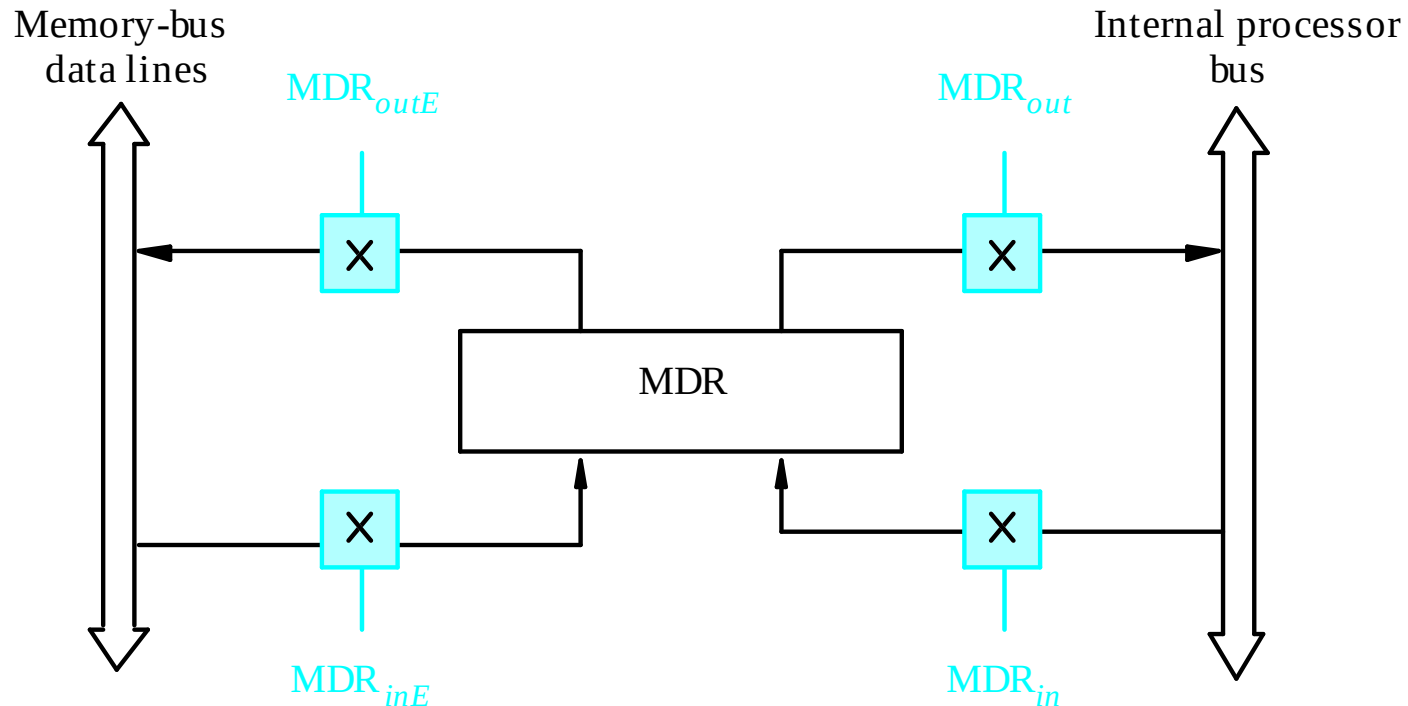


Figure 7.4. Connection and control signals for register MDR.

Functions of Components of Processor

- ALU
 - performs arithmetic and logic operations on data values stored in registers or memory
- CU (Control Unit)
 - generates all control signals to ensure the *sequence of all micro-operations (register/memory transfers/arithmetic or logic operations)* related to a machine code instruction
 - Activates the specific hardware units that are required for the set of operations that execution of a machine instruction requires
i.e. opcode **decoding**

Register Transfers

 


Figure 7.2. Input and output gating for the registers in Figure 7.1.

Micro-operation sequence and Control Signals for Fetching a Word from Memory

- The response time of each memory access varies (cache miss- memory-mapped I/O).
- To accommodate this, the processor waits(WMFC) until it receives from memory-a Memory-Function-Completed, MFC signal.

For Assembly code Instruction: MOV (R3),R1 (assuming R1 is destination

Time	(ActionsNeeded) Micro-operations	Control Unit needs to generate following Control Signals
T1:	MAR<- [R3]	R3out, MARin, Read (starts a read signal on memory bus)
T2:	Load MDR from memory bus when MFC received	MDRinE, WMFC
T2+n :	R1 <- [MDR]	MDRout, R1in

Register Transfers

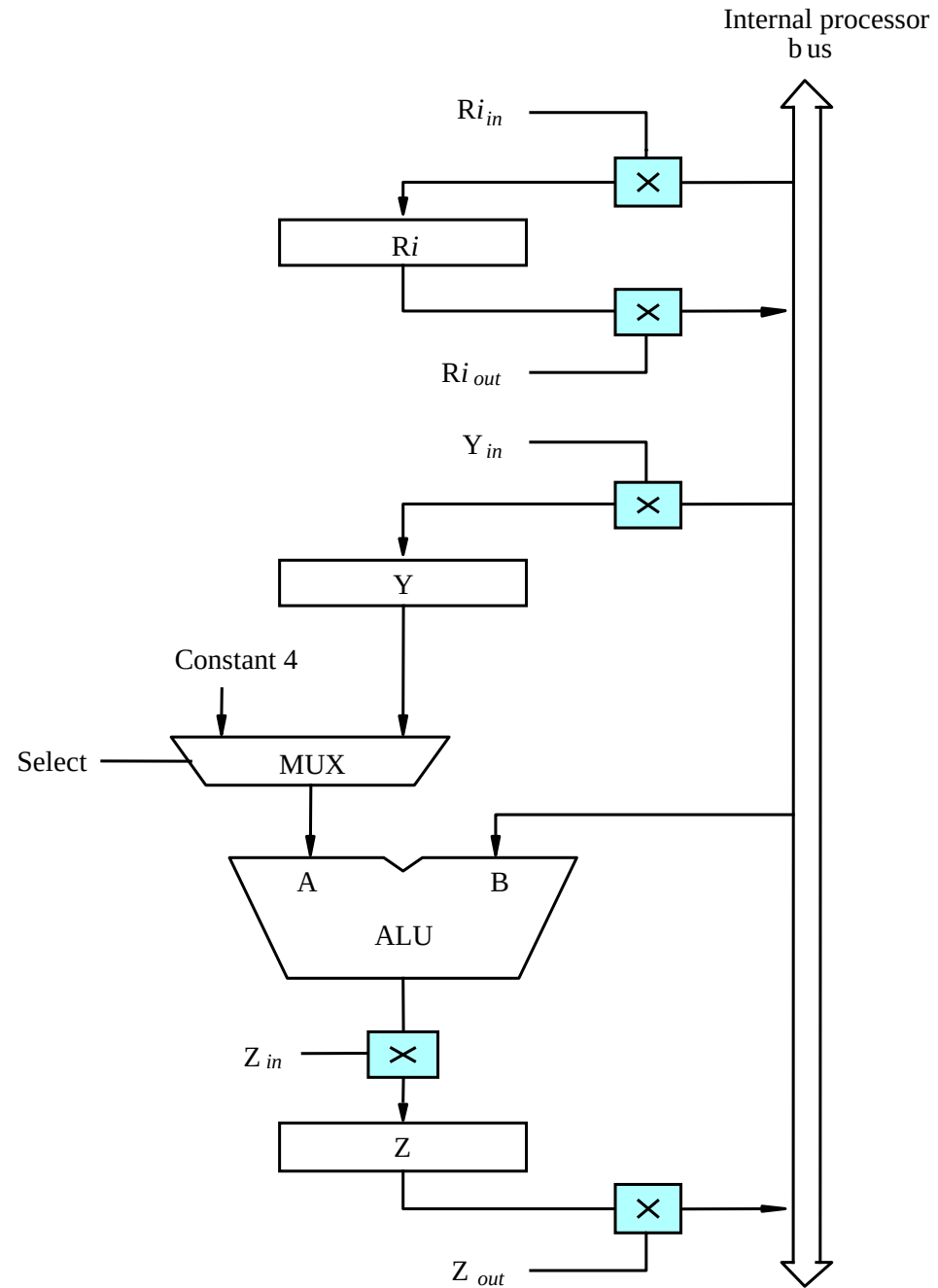



Figure 7.2. Input and output gating for the registers in Figure 7.1.

Performing an Arithmetic or Logic Operation

- The ALU is a combinational circuit that has no internal storage.
- ALU gets the two operands from MUX and bus. The result is temporarily stored in register Z.

For Assembly code `ADD R1,R2,R3` `//R3`
 destination

Time	(Actions Needed) Micro-operations	Control Signals Needed
T1:	$Y \leftarrow R1$	$R1_{out}$, Y_{in}
T2:	$Z \leftarrow R2 + Y$	$R2_{out}$, $SelectY$, Add , Z_{in}
T3:	$R3 \leftarrow Z$	Z_{out} , $R3_{in}$

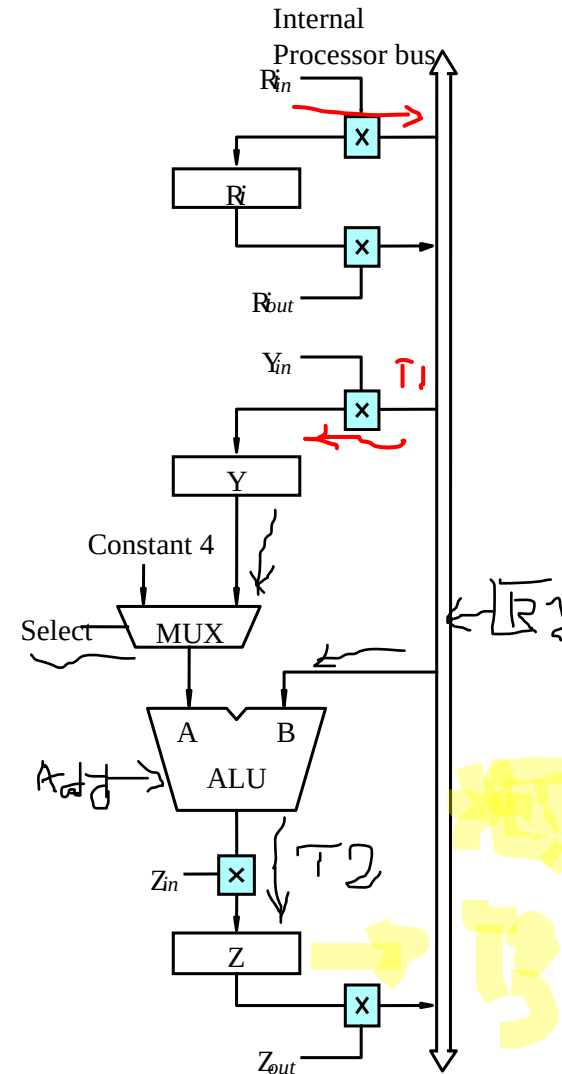

Input and output gating for the registers in Figure 7.1.

Execution of another Assembly/M/C Instruction

Add (R3), R1

Step	Action
1	PC _{out} , MAR _{in} , Read, Select4Add, Z _{in}
2	Z _{out} , PC _{in} , Y _{in} , WMFC
3	MDR _{out} , IR _{in}
4	R3 _{out} , MAR _{in} , Read
5	R1 _{out} , Y _{in} , WMFC
6	MDR _{out} , SelectY, Add, Z _{in}
7	Z _{out} , R1 _{in} , End

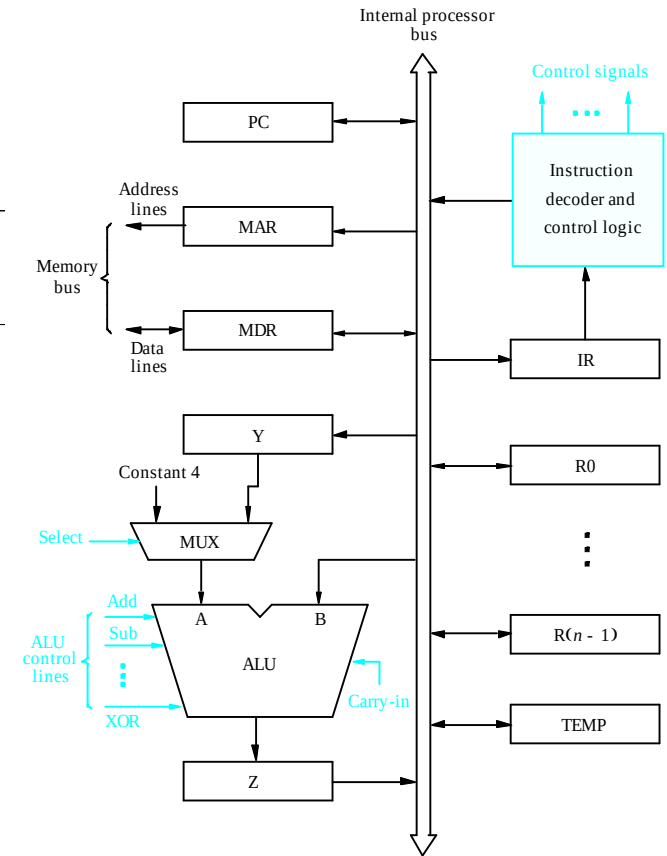


Figure 7.1. Single-bus organization of the datapath inside a processor.

Figure 7.6. Control sequence for execution of the instruction Add (R3), R1.

Execution of Branch Instructions

- A branch instruction replaces the contents of PC with the branch target address, which is usually obtained by adding an offset X given in the branch instruction.
- The offset X is usually the difference between the branch target address and the address immediately following the branch instruction.
- Conditional branch

Execution of Branch Instructions

Step	Action
------	--------

- | | |
|---|---|
| 1 | PC_{out} , MAR_{in} , Read, Select 4, Add, Z_{in} |
| 2 | Z_{out} , PC_{in} , Y_{in} , WMF C |
| 3 | MDR_{out} , IR_{in} |
| 4 | Offset-field-of- IR_{out} , Add, Z_{in} |
| 5 | Z_{out} , PC_{in} , End |
-

Figure 7.7. Control sequence for an unconditional branch instruction.

Quiz

- What is the control sequence for execution of the instruction

Add R1, R2

including the instruction fetch phase? (Assume single bus architecture)


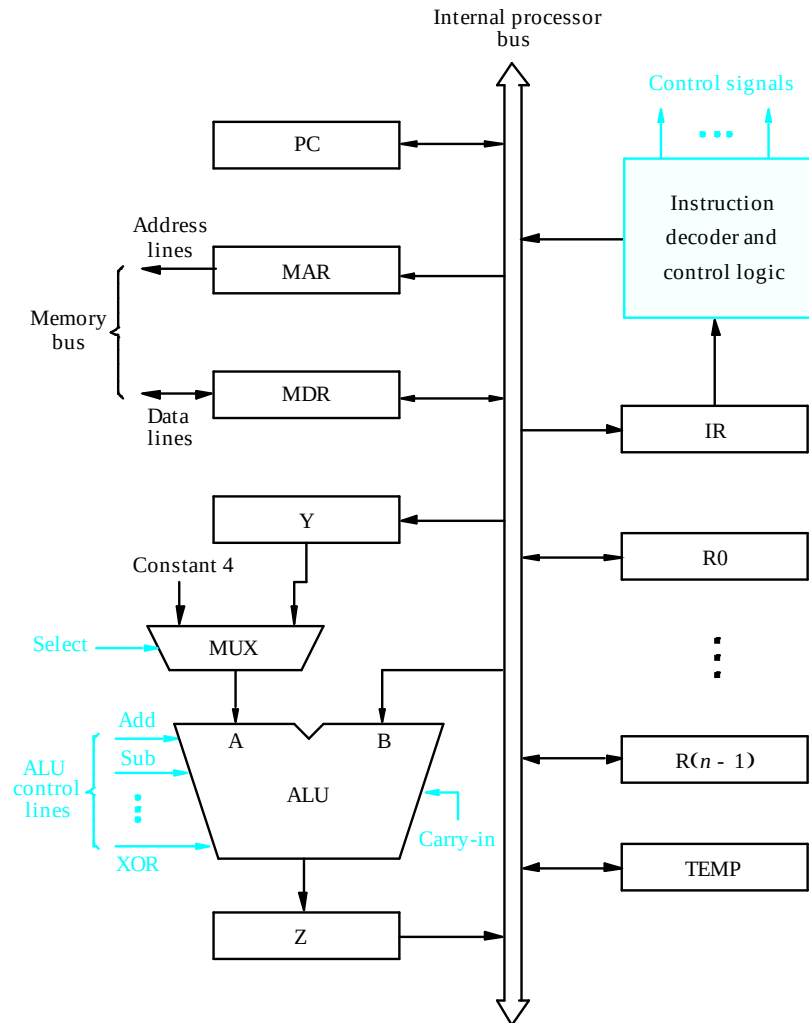


Figure 7.1. Single-bus organization of the datapath inside a processor.

Notice the states are finite in number

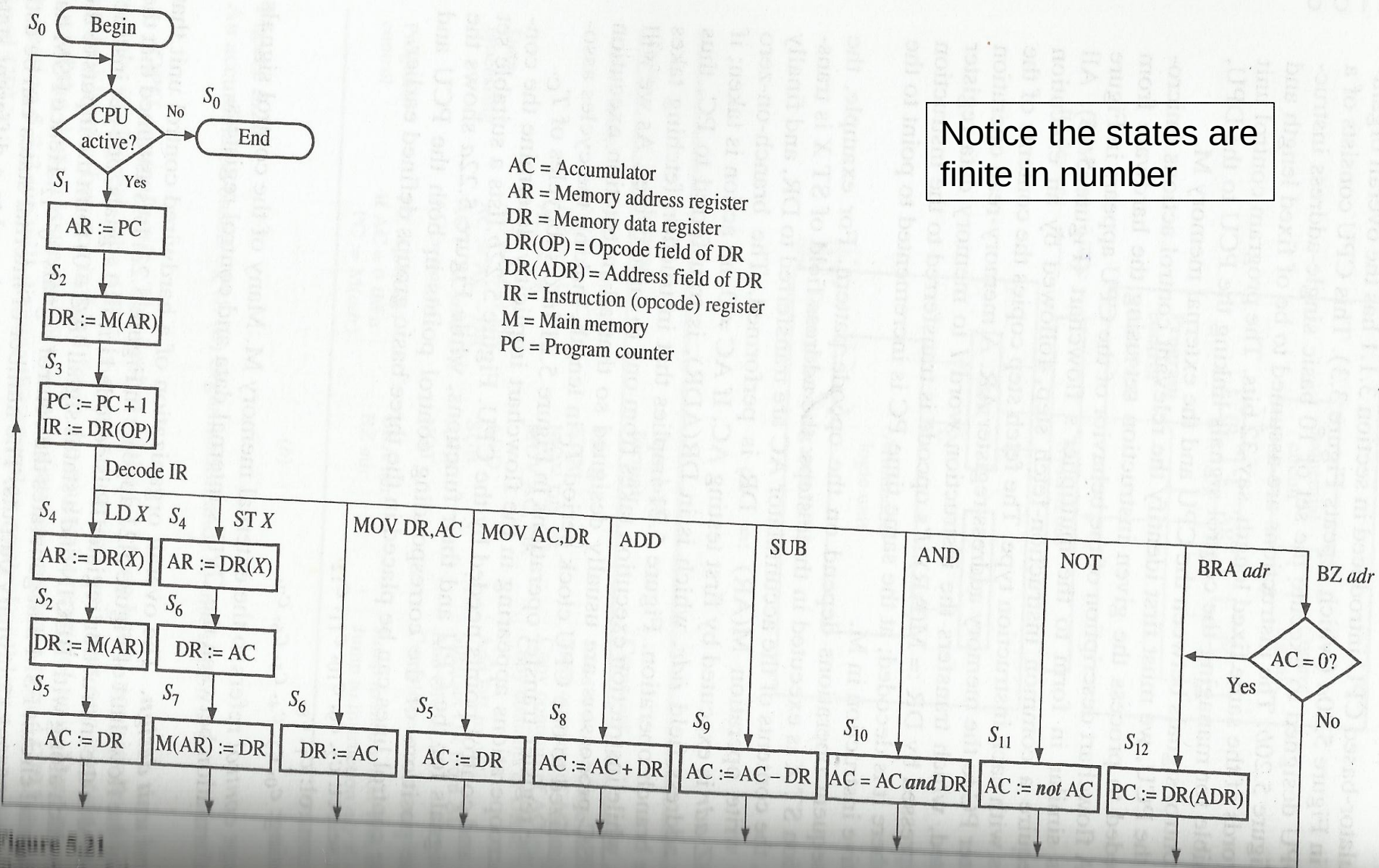

Hardwired Control

Processor (Control Unit)Overview

- To execute instructions, the processor must have some means of generating the control signals needed in the proper sequence.
- Two categories: **hardwired control** and **microprogrammed control**
- Hardwired system can operate at high speed; but with little flexibility.

Control Unit Organization

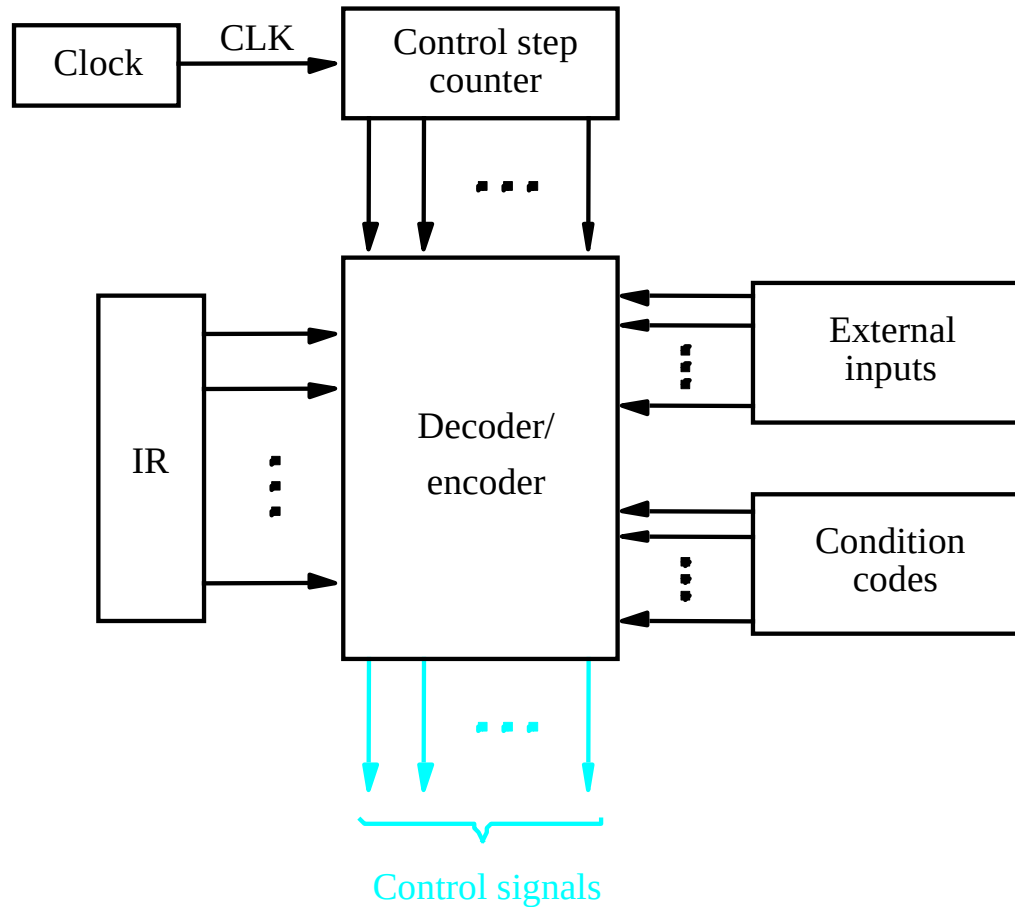


Figure 7.10. Control unit organization.

Detailed Block Description

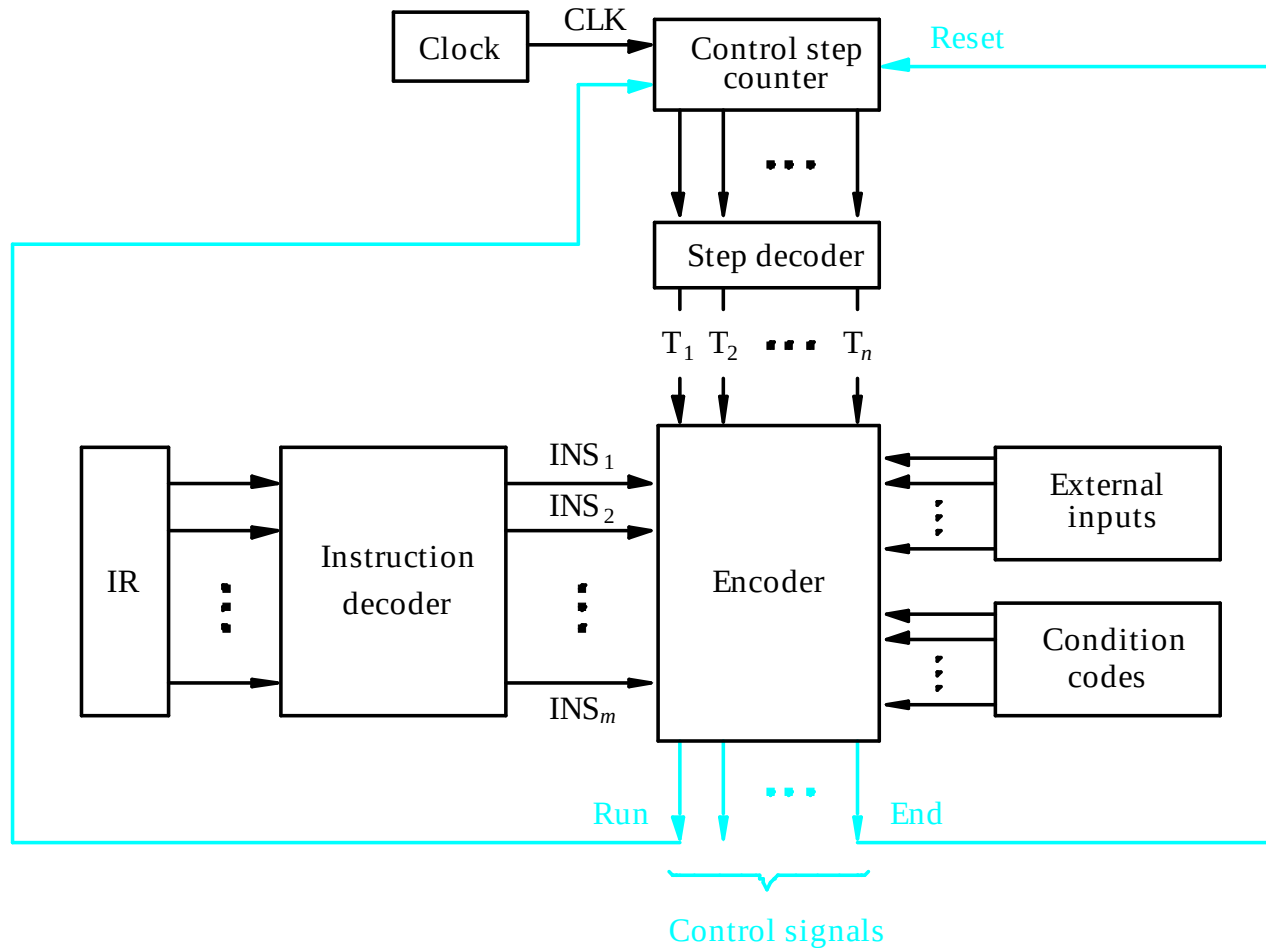


Figure 7.11. Separation of the decoding and encoding functions.


Hardwired Control Unit (for our simple example)

From Malvino

Op Mode Decoder

Control Step Counter

Digital Computer Electronics

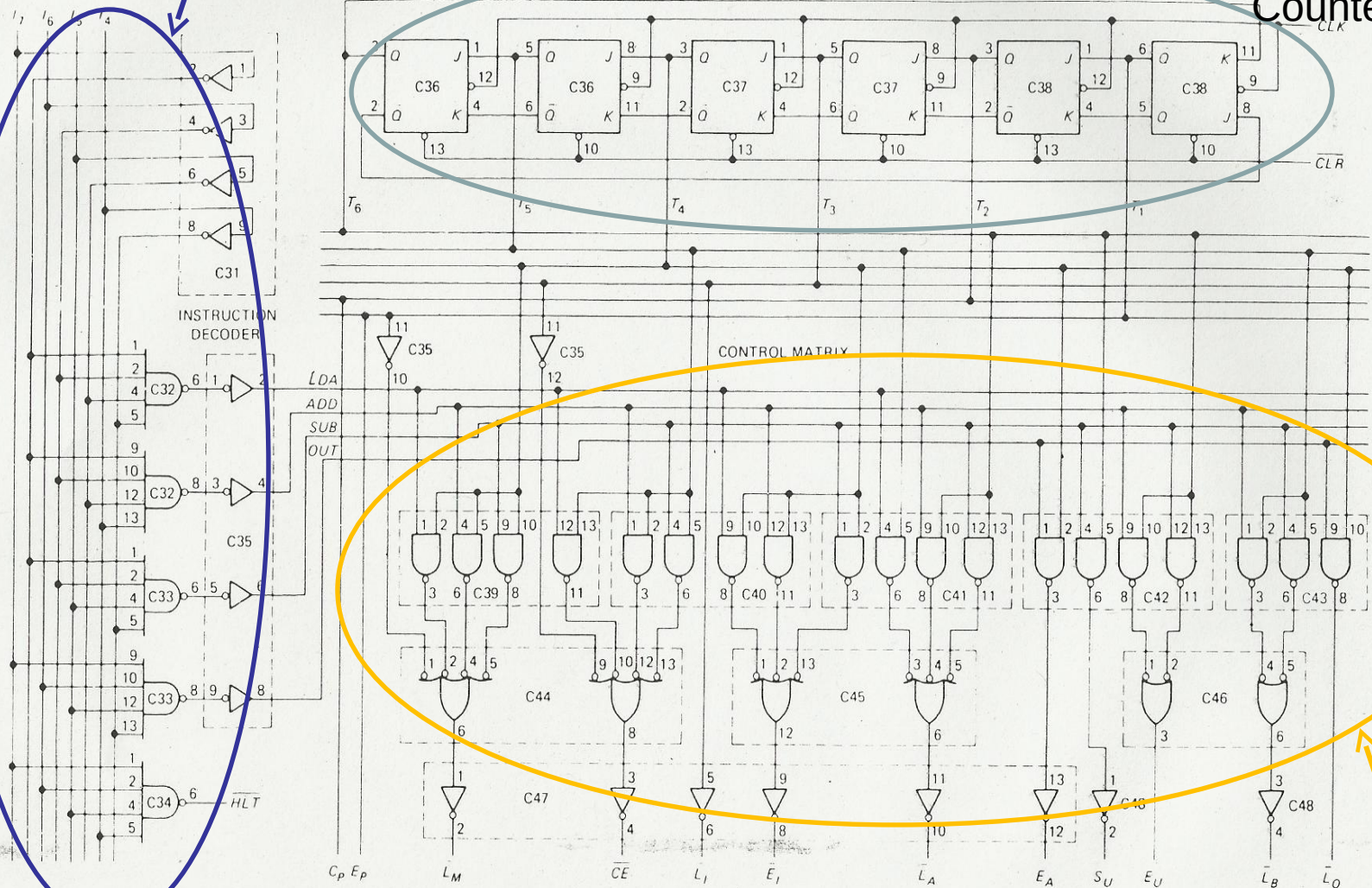


Encoder

Fig. 10-15 Instruction decoder, ring counter, and control matrix.

From
Malvino

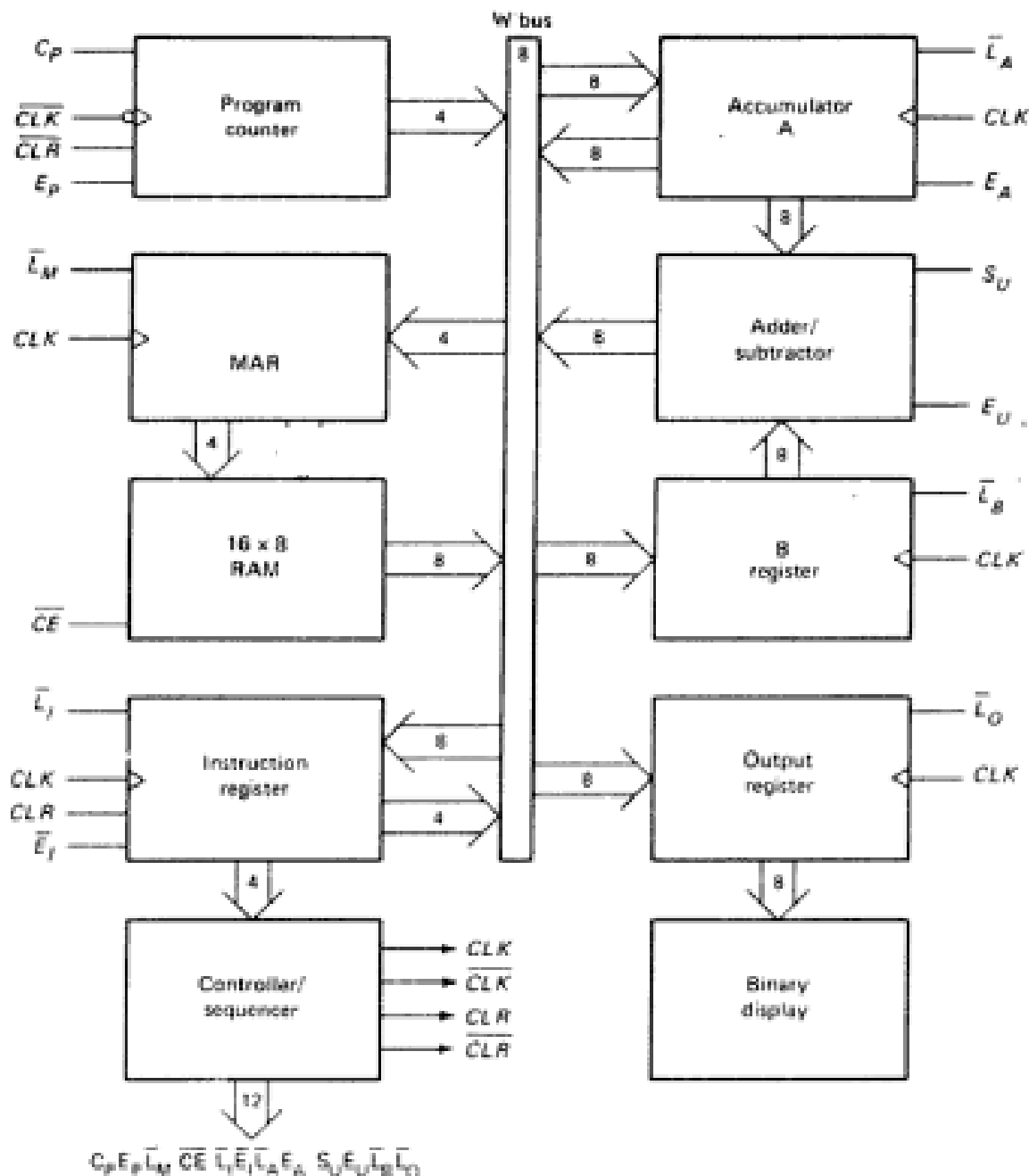No input
from
outside:
It is
assumed
all instruction
and data
already
stored in
RAM.



- The above 2 slides are just to illustrate what goes into the blocks (shown in the detailed block description slide) for a very simple processor with Single bus Organization of Datapath
 - NOT for your exam purposes

Generating Z_{in}

- $Z_{in} = T_1 + T_6 \cdot \text{ADD} + T_4 \cdot \text{BR} + \dots$

 



Figure 7.12. Generation of the Z_{in} control signal for the processor in Figure 7.1.

Performing an Arithmetic or Logic Operation

- The ALU is a combinational circuit that has no internal storage.
- ALU gets the two operands from MUX and bus. The result is temporarily stored in register Z.

For Assembly code `ADD R1,R2,R3` //R3
destination

Time	(Actions Needed) Micro-operations	Control Signals Needed
T _n :	Y ← R1	R1out, Yin
T _{n+1} :	Z ← R2 + Y	R2out, SelectY, Add, Zin
T _{n+2} :	R3 ← Z	Zout, R3in

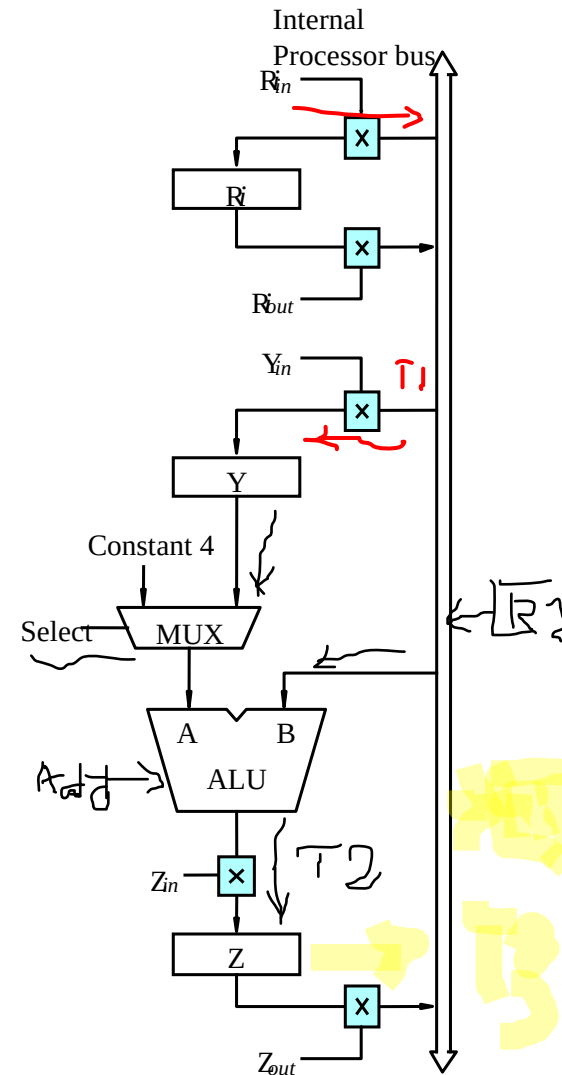

Input and output gating for the registers in Figure 7.1.

Generating End

- $\text{End} = T_7 \cdot \text{ADD} + T_5 \cdot \text{BR} + (T_5 \cdot N + \overline{T_4} \cdot N) \cdot \text{BRN} + \dots$


 


Figure 7.13. Generation of the End control signal.

 States of a Simple Accumulator based Processor from Hayes Page 328



Describe how the processor generates the control signals needed in the proper sequence to execute instructions using following Detailed Block Description of Hardware

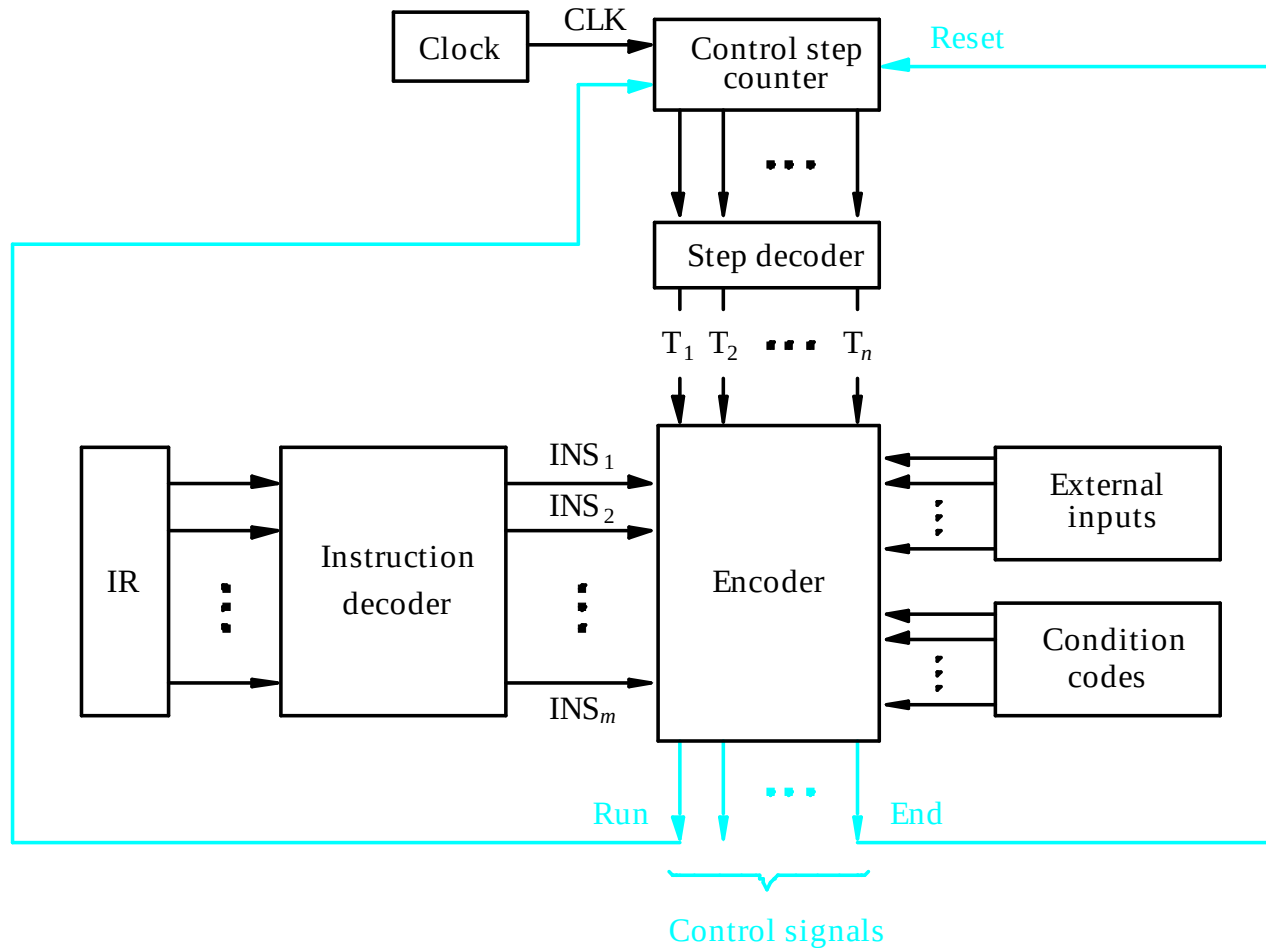


Figure 7.11. Separation of the decoding and encoding functions.

Microprogrammed Control Unit

- Control signals are generated by a program similar to machine language programs.
- Control Word (CW); microroutine; microinstruction


Micro - instruction	;	PC _{in}	PC _{out}	MAR _{in}	Read	MDR _{out}	IR _{in}	Y _{in}	Select	Add	Z _{in}	Z _{out}	R1 _{out}	R1 _{in}	R3 _{out}	WMFC	End	;
1		0	1	1	1	0	0	0	1	1	1	0	0	0	0	0	0	
2		1	0	0	0	0	0	1	0	0	0	1	0	0	0	1	0	
3		0	0	0	0	1	1	0	0	0	0	0	0	0	0	0	0	
4		0	0	1	1	0	0	0	0	0	0	0	0	0	1	0	0	
5		0	0	0	0	0	0	1	0	0	0	0	1	0	0	1	0	
6		0	0	0	0	1	0	0	0	1	1	0	0	0	0	0	0	
7		0	0	0	0	0	0	0	0	0	0	1	0	1	0	0	1	

Figure 7.15 An example of microinstructions for Figure 7.6.

Reference-Fig 7.5 in previous slide

- 1 control word(CW) is 1 row of above table
 - Each bit responsible for Activating some micro-operations
 - 1 CW contains 1 micro-instruction.
- 7 microinstructions in Fig 7.5 called micro-routine
- All micro-routines required to code a computer instruction set are stored on **control memory** ROM

 States of a Simple Accumulator based Processor from Hayes Page 328



Control Sequencer

- Sends out control words (16 bit in example)
 - One during each T state or clock cycle
- Each is a microinstruction , stored in control memory(ROM)
- Each bit of these 16 bits 1 s and 0s are the set of control signals required for all the microoperations(register input/output enable,arithmetic/login operation) required at that state.

Control Memory(ROM)

Fetch

Address	Control Word
0 H
1 H
2H
3H
4H
5H
6H	.
7H	.
8H	.


Address ROM

Op Code	Starting Address
0000 (LDA)	0011
0001 (ADD)	0110
0010 (SUB)	1001

	.
	.
	.

Next Address Decision

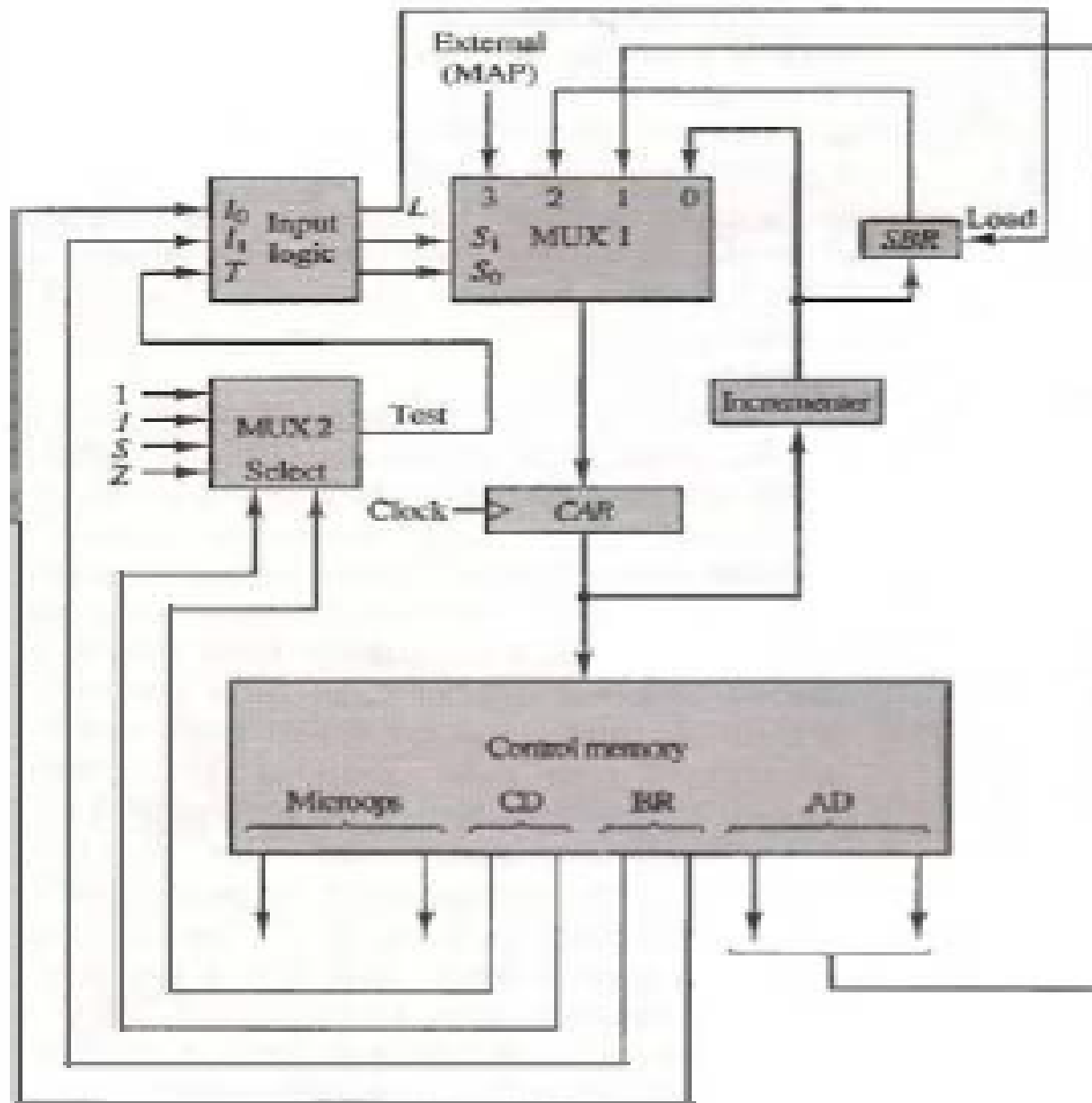- Depending on ALU flags and control buffer register:
 - Get next instruction
 - Add 1 to control address register
 - Jump to new routine based on jump microinstruction
 - Load address field of control buffer register into control address register
 - Jump to machine instruction routine
 - Load control address register based on opcode in IR



MUX1		
S1	S0	L
0	0	
0	1	
1	0	
1	1	1

Figure 7-8 Microprogram sequencer for a control memory.

Control Memory(ROM)

Fetch

Address	Control Word
0 H
1 H
2H
3H
4H
5H
6H	.
7H	.
8H	.

Address ROM


Op Code	Starting Address
0000 (LDA)	0011
0001 (ADD)	0110
0010 (SUB)	1001

	.
	.
	.

Horizontal Versus Vertical Microcode Schemes

- In horizontal microcode, each control signal is represented by a bit in the μ instruction
 - Fewer control store words of more bits per word
- In vertical microcode, a set of true control signals is represented by a shorter code
 - Vertical μ code only allows RTs in a step for which there is a vertical μ instruction code
 - Thus vertical μ code may take more control store words of fewer bits

 Completely Horizontal and Vertical Microcoding



Horizontal Micro-programming

- Wide control memory word
- High degree of parallel operations possible
- Little encoding of control information
- Fast

Vertical Micro-programming

- Width can be much narrower
- Control signals encoded into function codes – need to be decoded
- More complex, more complicated to program, less flexibility
- More difficult to modify
- Slower

Difference between
Hardwired Control Unit Processor
and
Microprogrammed Control Unit Processor

Hardwired Control system

- Advantage
 - can operate at high speed (RISC)
- Disadvantage:
 - Hardware error : difficult to rectify
 - Too complex instruction set – impossible to implement
 - Not easy to modify(very little flexibility)

Microprogrammed Control System

- Advantage:
 - Simplifies design of control unit
 - Cheaper
 - Less error-prone
 - Easier to modify (CISC)
- Disadvantage:
 - Slower

Practice Exercises: Control Unit

1. State the difference between Hardwired Control Unit Processor and Microprogrammed Control Unit Processor.
2. Explain using block diagram the functioning of a
 - a. hardwired control unit
 - b. microprogrammed control unit

Practice Exercises: Control Unit

3. Explain with a block diagram how the next address for the control word to be fetched is found using a MUX.
4. Given a control memory of size 2048 and word size of 12 bits, how many bits each will be the 4 addresses that go into the MUX ?