

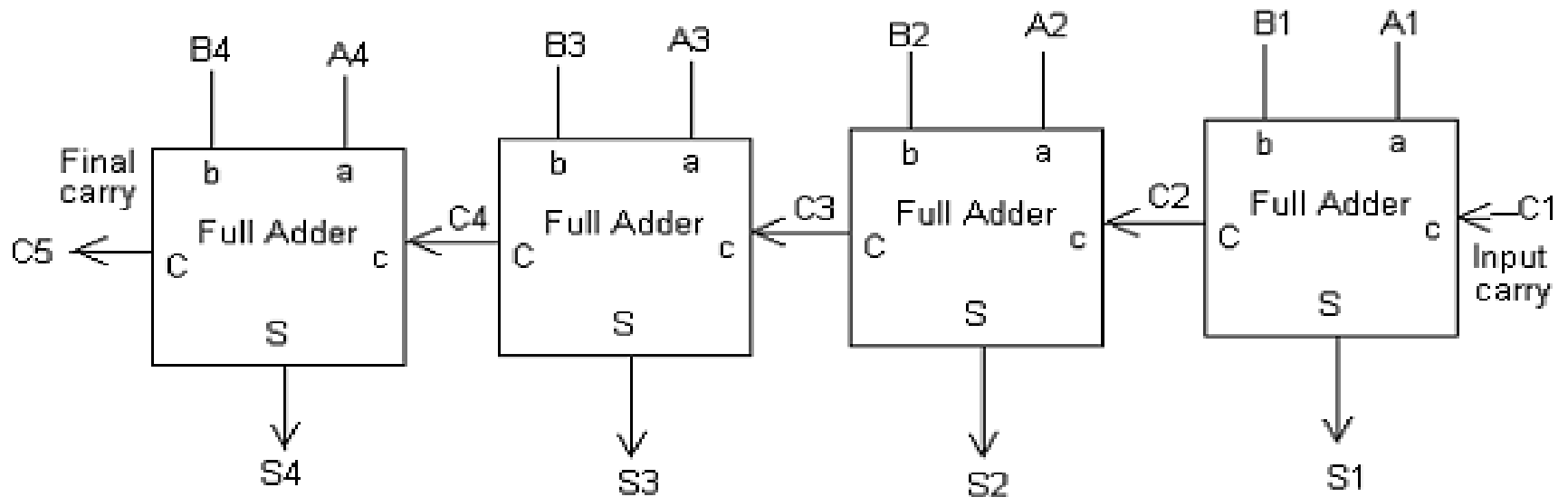


Parallel Adder: Ripple Carry Adder

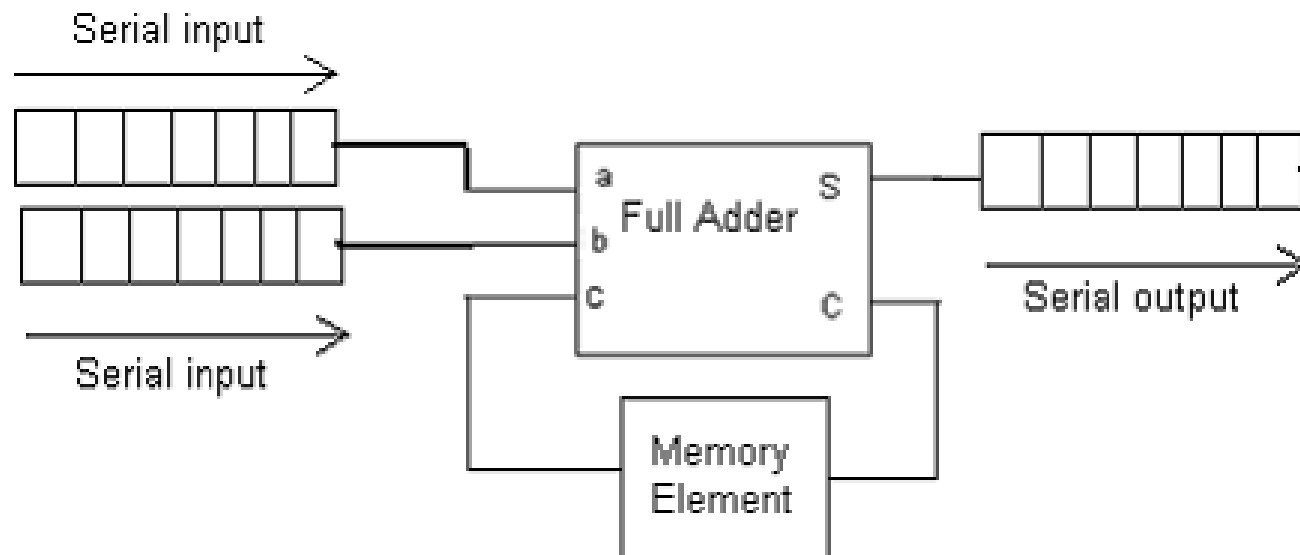(Carry Look-ahead adders also is parallel adder)



Serial Adder

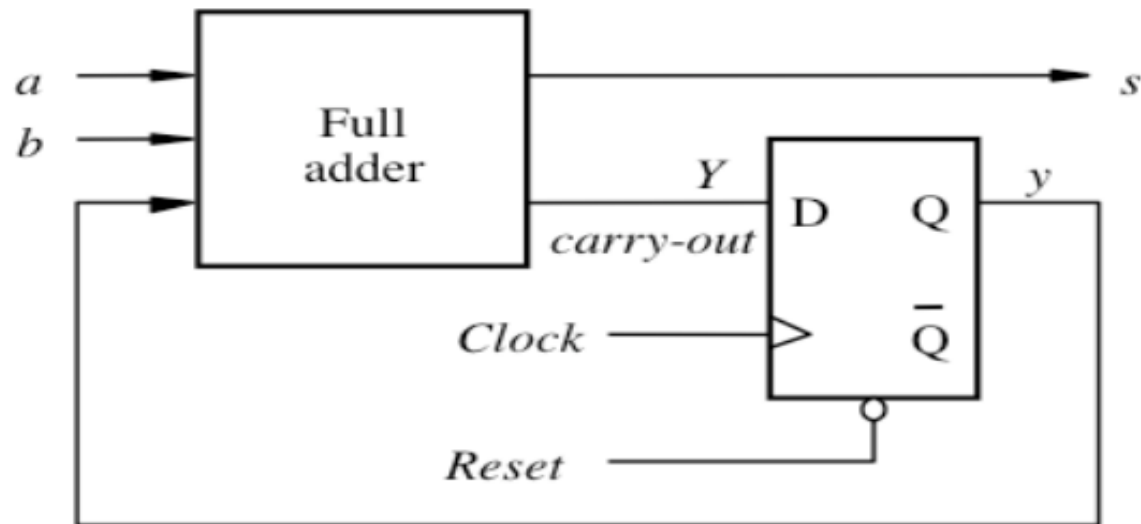

Multiplication

- 1. For unsigned/positive integers

Sequential Circuit Binary Multiplier

(based on multiplication by hand)

1101---M (Multiplicand) (+13) 4bit

1011---Q (Multiplier) (+11) x 4bit

1101 1101x2⁰ x1 8 bits at

most

1101 1101x2¹ x1

0000 1101x2² x 0


11 01 1101x2³ x 1

10001111 (143)

4bit x4bit multiplication need 4bit
adder repeat addshift /shift 4 times

C		1101	M	Q		Initial State	13
0		0000	A	1011			11
0		1101			Add M	Cycle 1	
0		1101		1011			
0		0110		1101	Shift		
0		1101		1101	Add	Cycle 2	
1		0011		1101			
0		1001		1110	Shift		
0		0100		1111	Shift	Cycle 3	
0		1101		1111	Add M		
1		0001		1111		Cycle 4	
0		1000		1111	Shift		143

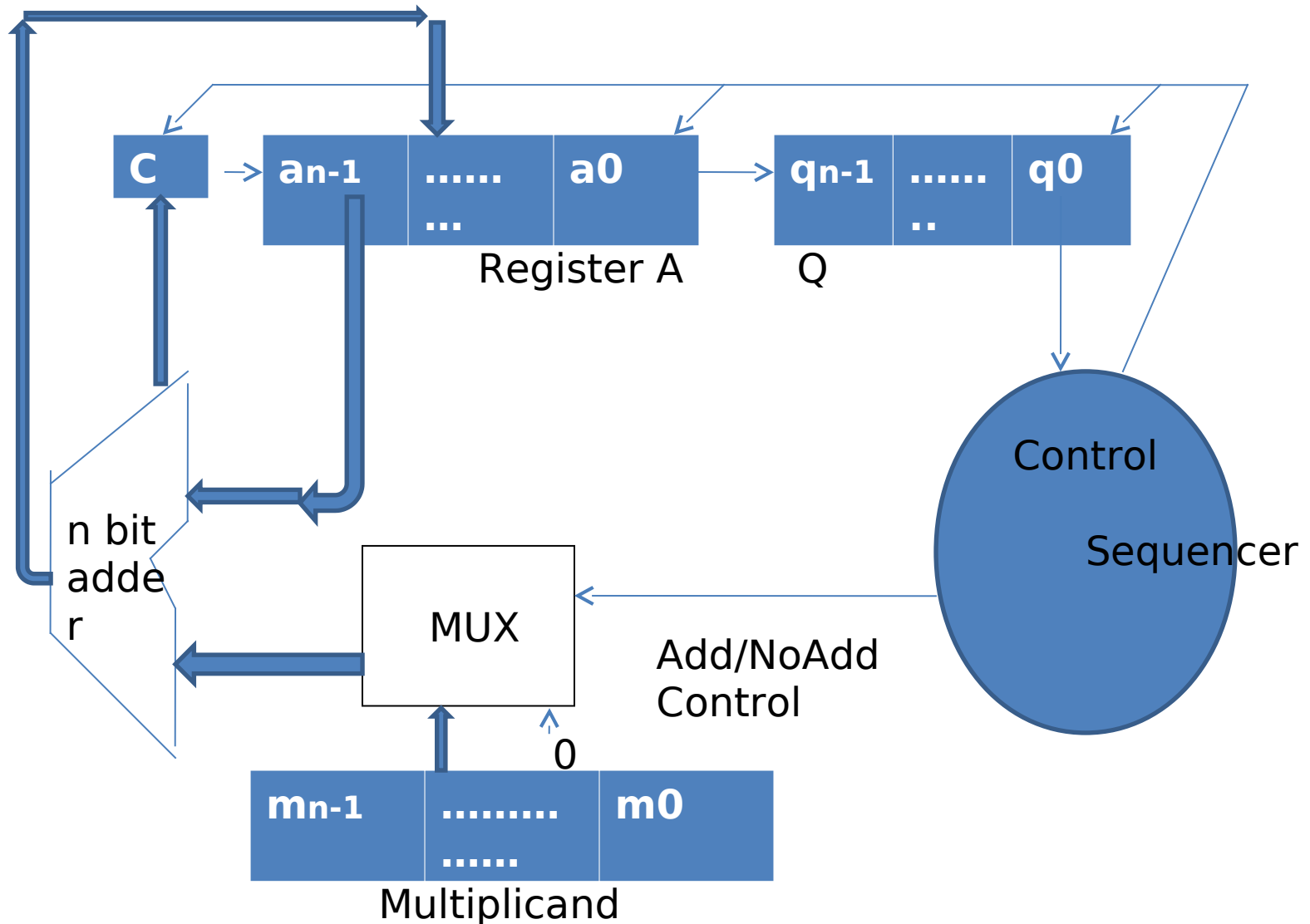Register Configuration Sequential Circuit



Multiplication

- 2. For signed number in 2's complement

Booth Algorithm

Facts used in this algorithm

$$Q=001110 = 2^3 + 2^2 + 2^1 = +14 = 2^4 - 2^1$$

$$M \times Q = M \times 2^4 - M \times 2$$

M (Multiplicand) 4bit

Q (Multiplier) x 4bit

8 bits product


4 cycles to finish calculation

Sign extension needed to keep track of sign

Booth's Algorithm $M \times Q = 7 \times 3$

A	Q	Q ₋₁	M	-M	Initial State	7
0000	0011	0	0111	1001	Cycle 1	3
1001	0011	0	A-M			
1001	0011	0				
1100	1001	1	Arithmetic Right Shift		Cycle 2	
1110	0100	1	ARS			
0111	0100	1	A+M			
0101	0100	1	ARS		Cycle 3	
0010	1010	0				
0001	0101	0				
Prod	uct				Cycle 4	21

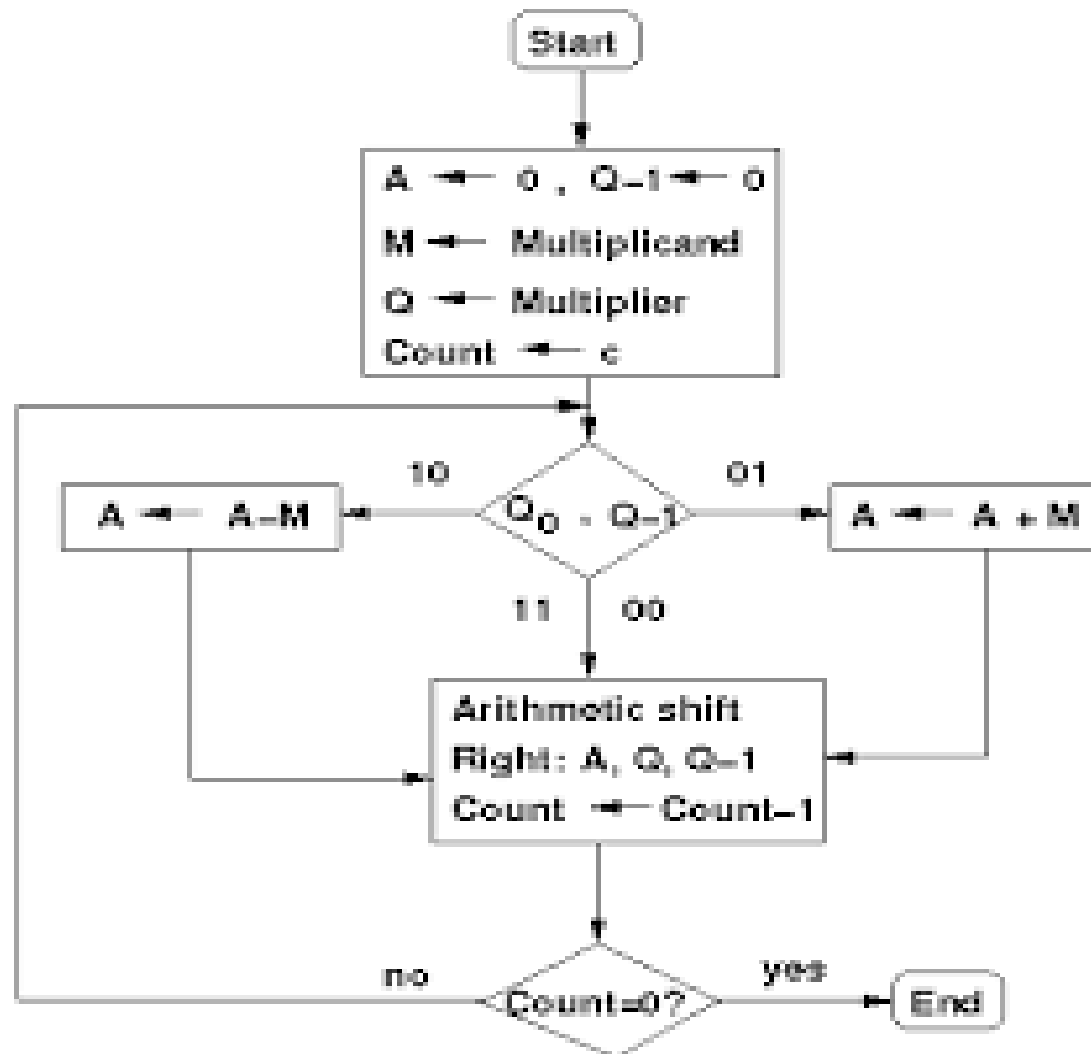Flowchart of Multiplication using Booth's Algorithm



Multiplication (13 x -6) using Booth's Algorithm

$$\begin{array}{r}
 01101 \quad (+13) \\
 \times 11010 \quad (-6) \\
 \hline
 \end{array}$$




$$\begin{array}{r}
 01101 \\
 0-1+1-10 \\
 \hline
 00000 \quad 00000 \\
 11111 \quad 0011 \\
 00001 \quad 101 \\
 11100 \quad 11 \\
 00000 \quad 0 \\
 \hline
 1110110010 \quad (-78)
 \end{array}$$

Multiplier bit-pair		Multiplier bit on the right $i - 1$	Multiplicand selected at position i
$i + 1$	i		
0	0	0	$0 \times M$
0	0	1	$+1 \times M$
0	1	0	$+1 \times M$
0	1	1	$+2 \times M$
1	0	0	$-2 \times M$
1	0	1	$-1 \times M$
1	1	0	$-1 \times M$
1	1	1	$0 \times M$

(b) Table of multiplicand selection decisions

Figure 6.14 Multiplier bit-pair recoding.

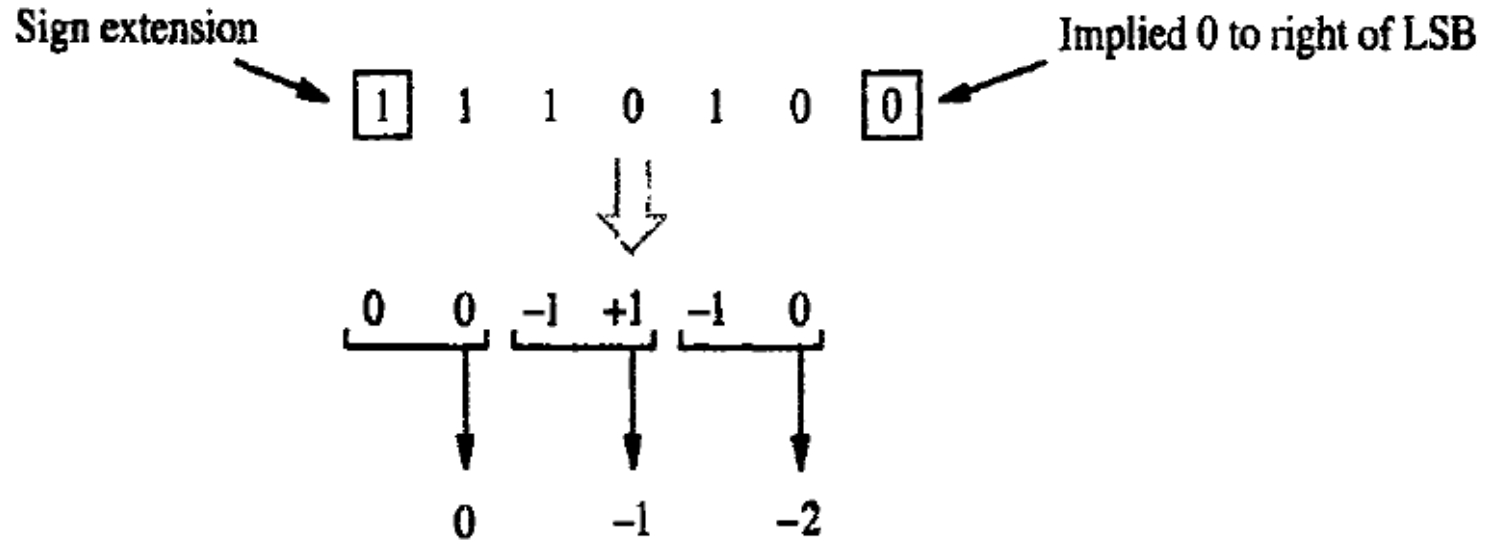Bit-pair Recoding of (-6) using Booth Recoding



(a) Example of bit-pair recoding derived from Booth recoding

Multiplication (13 x -6) using bit-pair recoding of Multipliers using Booth Recoding

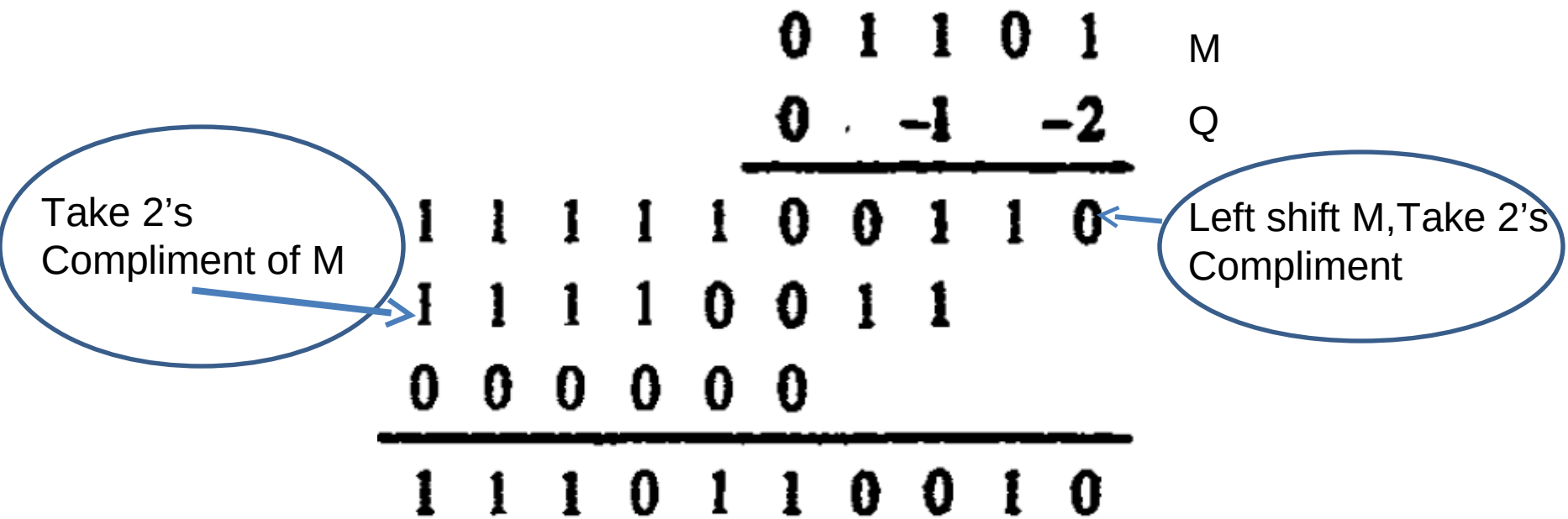


Figure 6.15 Multiplication requiring only $n/2$ summands.