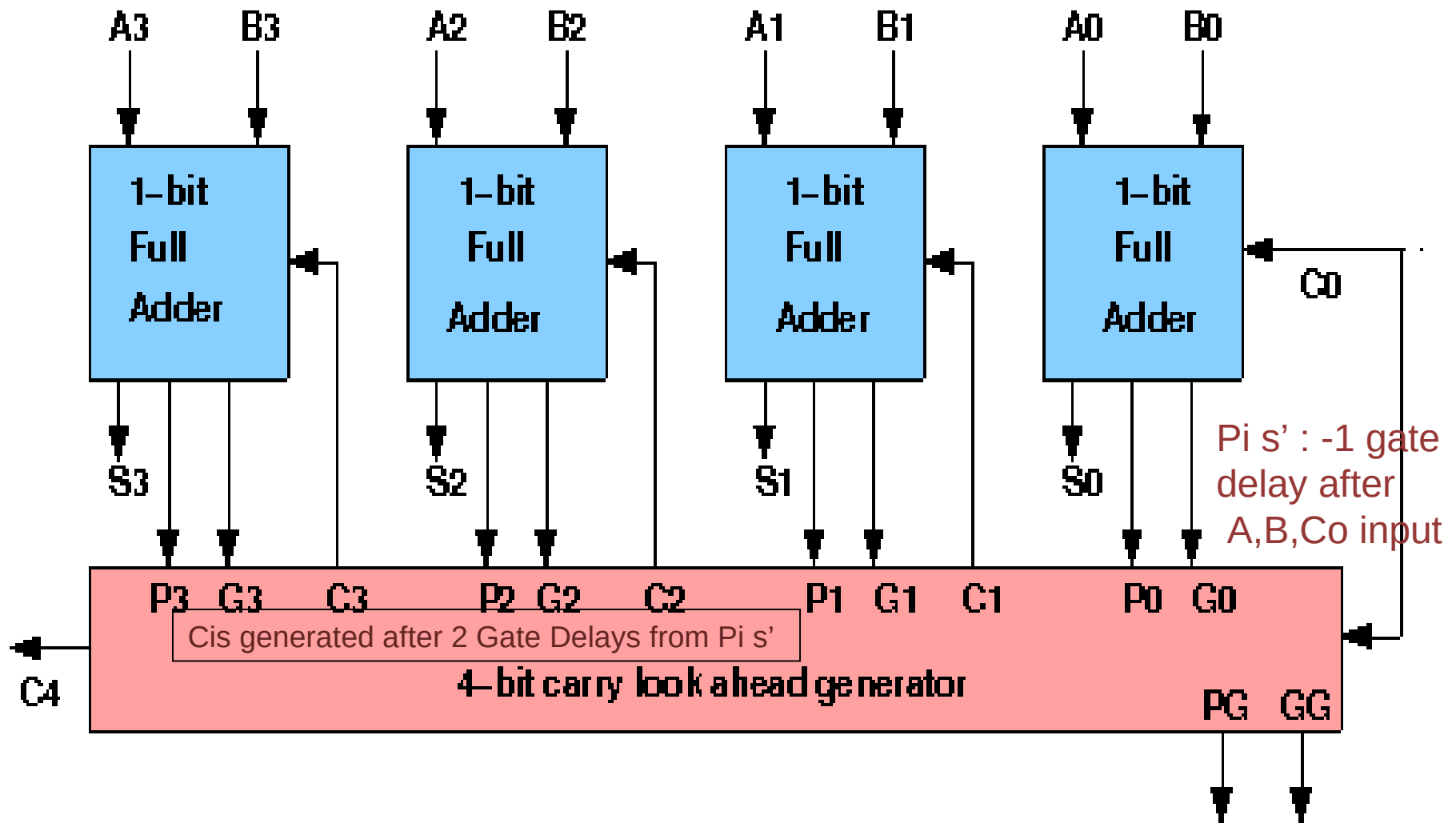


Design of Carry Lookahead Adders

- To reduce the computation time
 - faster ways to add two binary numbers by using carry lookahead adders.
 - creating two signals P (**Carry Propagator**) and G (**Carry Generator**). The block diagram of a 4-bit Carry Lookahead Adder is shown in next slide



- $\text{Sum}_i = A_i \oplus B_i \oplus C_i$
- $C_{i+1} = A_i \cdot B_i + (A_i \oplus B_i) C_i$

Replace by

- $P_i = A_i \oplus B_i$
- $G_i = A_i \cdot B_i$
- The output sum and carry can be expressed as
- $\text{Sum}_i = P_i \oplus C_i$
- $C_{i+1} = G_i + (P_i \cdot C_i)$

Boolean function for the carry output of each stage and substitute for each C_i its value from the previous equations:

- $C_1 = G_0 + P_0 \cdot C_0$
- $C_2 = G_1 + P_1 \cdot C_1 = G_1 + \underline{P_1 \cdot G_0} + \underline{P_1 \cdot P_0 \cdot C_0}$
- $C_3 = G_2 + P_2 \cdot C_2 = G_2 + \underline{P_2 \cdot G_1} + \underline{P_2 \cdot P_1 \cdot G_0} + \underline{P_2 \cdot P_1 \cdot P_0 \cdot C_0}$
- $C_4 = G_3 + P_3 \cdot C_3 = G_3 + P_3 \cdot G_2 + P_3 \cdot \underline{P_2 \cdot G_1} + P_3 \cdot \underline{P_2 \cdot P_1 \cdot G_0} + P_3 \cdot \underline{P_2 \cdot P_1 \cdot P_0 \cdot C_0}$

(Note: Five fan in gate is practical limit)

Logic diagram of carry look-ahead generator

- C_3 is propagated at the same time as C_2 and C_1 .


 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

 

Group Propagate and Group Generate Delay


- The Carry Look Ahead 4-bit adder can also be used in a higher-level circuit by having each CLA Logic circuit produce a propagate and generate signal to a higher-level CLA Logic circuit. The **group propagate** (PI_0) and **group generate** (GI_0) for a 4-bit CLA are:


$$PI_0 = P_3 \cdot P_2 \cdot P_1 \cdot P_0 \quad \text{1 gate level (and) after } P_i$$

$$GI_0 = G_3 + P_3 \cdot G_2 + P_3 \cdot P_2 \cdot G_1 + P_3 \cdot P_2 \cdot P_1 \cdot G_0$$

(2gate levels (and,or) after P_i and G_i)

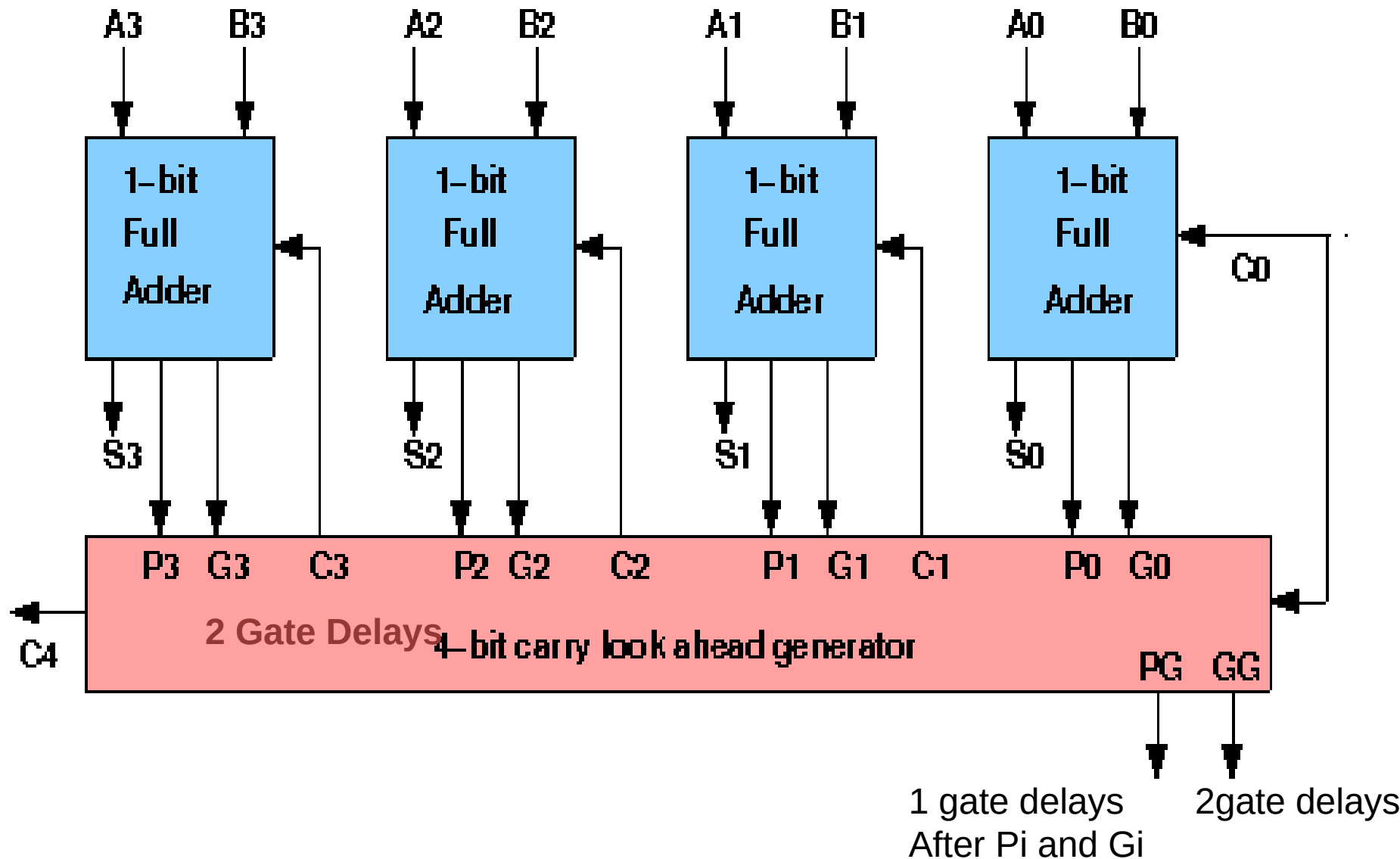All 4bit adder S_i - 4 gate delays, $PG=PI_0$
 All 4 bit adder C_i - 3 gate delays $GG=GI_0$



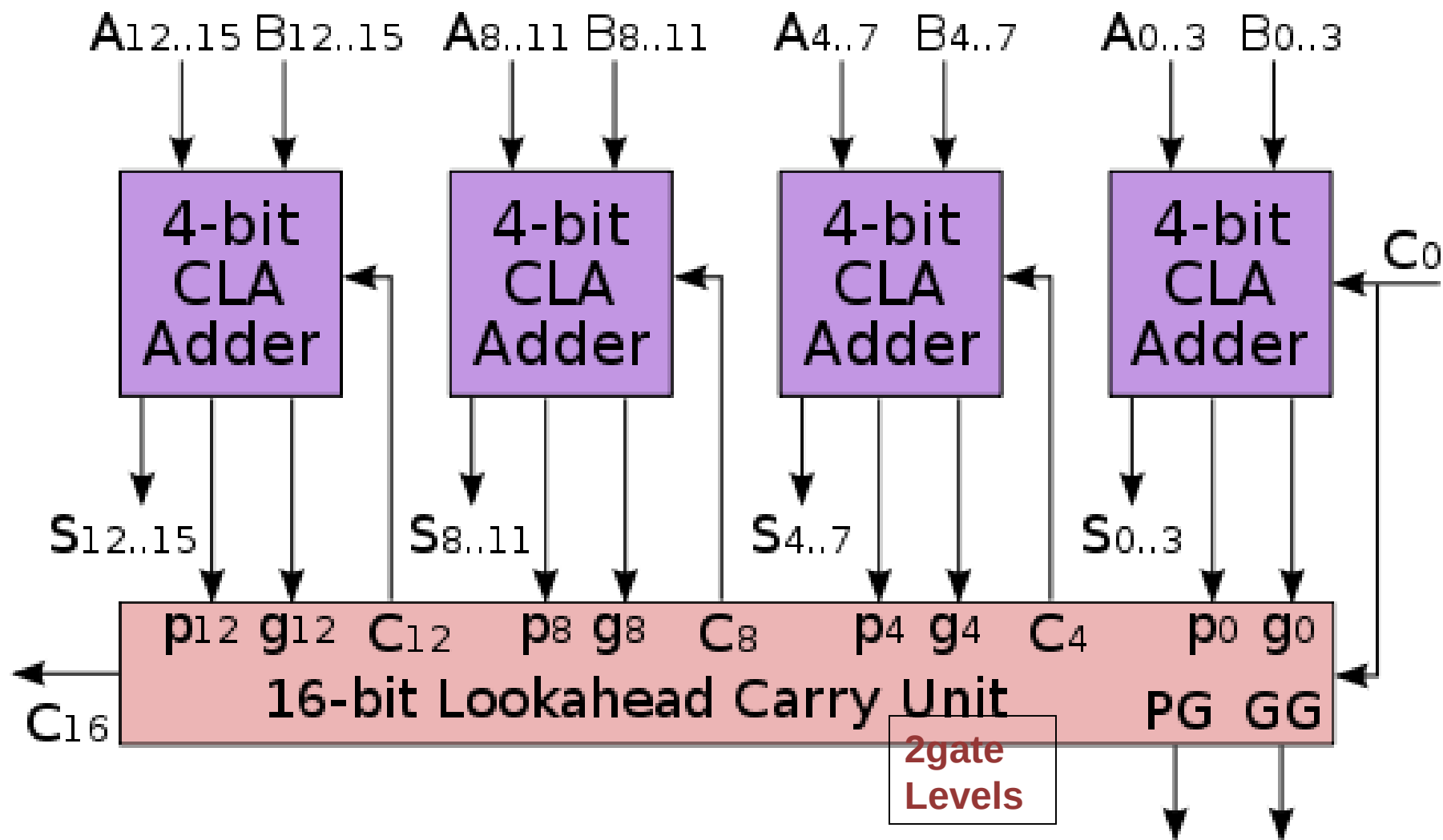

C4 to C12 : 5 gate delays, C_{15} : 2 more gate delays in 4bit CLA(5+2=7)

S15 .. S4 : 1 more gate delays= 1+7=8

Compare Carry Look Ahead to Ripple Carry

- The signal from input carry C_{in} to output carry C_{out} requires an AND gate and an OR gate
 - two gate levels.
- four full adders in the parallel adder, the output carry C_5 would have $2 \times 4 = 8$ gate levels from C_1 to C_5 . For an n -bit parallel adder, there are $2n$ gate levels to propagate through for **ripple carry adder**
- 16 bit ripple carry $2 \times 16 = 32$ gate delay