


Module No-2

Basics of ALU Design

Module No-2: Basics of ALU Design:

- Binary number representation;
- Fixed and Floating point representation of numbers.
- Adders: Serial and Parallel adders, Ripple Carry / Carry Look ahead / Carry Save;
- Multipliers & Divider Circuits: Multiplication of signed binary numbers Booth Multipliers;

ALU Inputs and Outputs

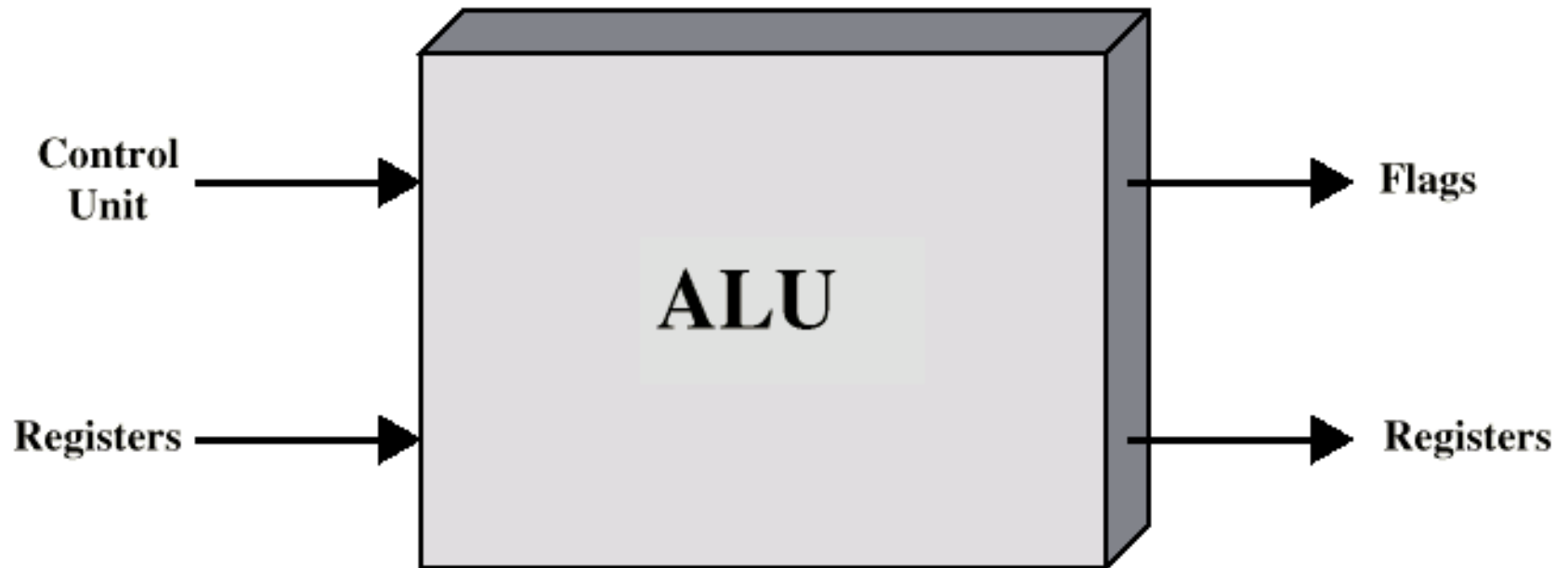

Integer Representation

- Only have 0 & 1 to represent everything
- Positive numbers stored in binary
 - e.g. 41=00101001
- No minus sign
- No period
- Sign-Magnitude
- Two's compliment

Sign-Magnitude

- Left most bit is sign bit
- 0 means positive
- 1 means negative
- $+18 = 00010010$
- $-18 = 10010010$
- Problems
 - Need to consider both sign and magnitude in arithmetic
 - Two representations of zero (+0 and -0)


Two's Complement

- $+3 = 00000011$
- $+2 = 00000010$
- $+1 = 00000001$
- $+0 = 00000000$
- $-1 = 11111111$
- $-2 = 11111110$
- $-3 = 11111101$


Benefits

- One representation of zero
- Arithmetic works easily (see later)
- Negating is fairly easy
 - $3 = 00000011$
 - Boolean complement gives 11111100
 - Add 1 to LSB 11111101

 Geometric Depiction of Twos Complement Integers



(a) 4-bit numbers

 

(b) n-bit numbers

Negation Special Case 1

- 0 = 00000000
- Bitwise not 11111111
- Add 1 to LSB +1
- Result 1 00000000
- Overflow is ignored, so:
- - 0 = 0 ✓

Negation Special Case 2

- $-128 = 10000000$
- bitwise not 01111111
- Add 1 to LSB $+1$
- Result 10000000
- So:
- $-(-128) = -128 \quad X$
- Monitor MSB (sign bit)
- It should change during negation

Range of Numbers

- 8 bit 2s compliment
 - $+127 = 01111111 = 2^7 - 1$
 - $-128 = 10000000 = -2^7$
- 16 bit 2s compliment
 - $+32767 = 01111111 11111111 = 2^{15} - 1$
 - $-32768 = 10000000 00000000 = -2^{15}$


Conversion Between Lengths

- Positive number pack with leading zeros
- $+18 = \quad\quad\quad 00010010$
- $+18 = 00000000\ 00010010$
- Negative numbers pack with leading ones
- $-18 = \quad\quad\quad 10010010$
- $-18 = 11111111\ 10010010$
- i.e. pack with MSB (sign bit)

Real Numbers


- Numbers with fractions
- Could be done in pure binary
 - $1001.1010 = 2^3 + 2^0 + 2^{-1} + 2^{-3} = 9.625$
- Where is the binary point?
- Fixed?
 - Very limited
- Moving?
 - How do you show where it is?

Floating Point

 

- $\pm \text{.significand} \times 2^{\text{exponent}}$
- Point is actually fixed between sign bit and body of mantissa
- Exponent indicates place value (point position)

Floating Point Examples

 

(a) Format

$$\begin{aligned}
 1.1010001 \times 2^{10100} &= 0 \ 10010011 \ 101000100000000000000000 = 1.638125 \times 2^{20} \\
 -1.1010001 \times 2^{10100} &= 1 \ 10010011 \ 101000100000000000000000 = -1.638125 \times 2^{20} \\
 1.1010001 \times 2^{-10100} &= 0 \ 01101011 \ 101000100000000000000000 = 1.638125 \times 2^{-20} \\
 -1.1010001 \times 2^{-10100} &= 1 \ 01101011 \ 101000100000000000000000 = -1.638125 \times 2^{-20}
 \end{aligned}$$

(b) Examples

Signs for Floating Point

- Mantissa is stored in 2s compliment
- Exponent is in excess or biased notation
 - e.g. Excess (bias) 128 means
 - 8 bit exponent field
 - Pure value range 0-255
 - Subtract 128 to get correct value
 - Range -128 to +127

Normalization

- FP numbers are usually normalized
- i.e. exponent is adjusted so that leading bit (MSB) of mantissa is 1
- Since it is always 1 there is no need to store it
- (c.f. Scientific notation where numbers are normalized to give a single digit before the decimal point e.g. 3.123×10^3)


FP Ranges

- For a 32 bit number
 - 8 bit exponent
 - $\pm 2^{256} \approx 1.5 \times 10^{77}$
- Accuracy
 - The effect of changing lsb of mantissa
 - 23 bit mantissa $2^{-23} \approx 1.2 \times 10^{-7}$
 - About 6 decimal places


IEEE 754

- Standard for floating point storage
- 32 and 64 bit standards
- 8 and 11 bit exponent respectively
- Extended formats (both mantissa and exponent) for intermediate results

IEEE 754 Formats

 


(a) Single format

 

 
(b) Double format

IEEE 754 Formats

- Most of the binary floating-point representations follow the IEEE-754 standard.
- The data type float uses IEEE 32-bit single precision format and the data type double uses IEEE 64-bit double precision format.
- A floating-point constant is treated as a double precision number by GCC.



Single Precession (32-bit)

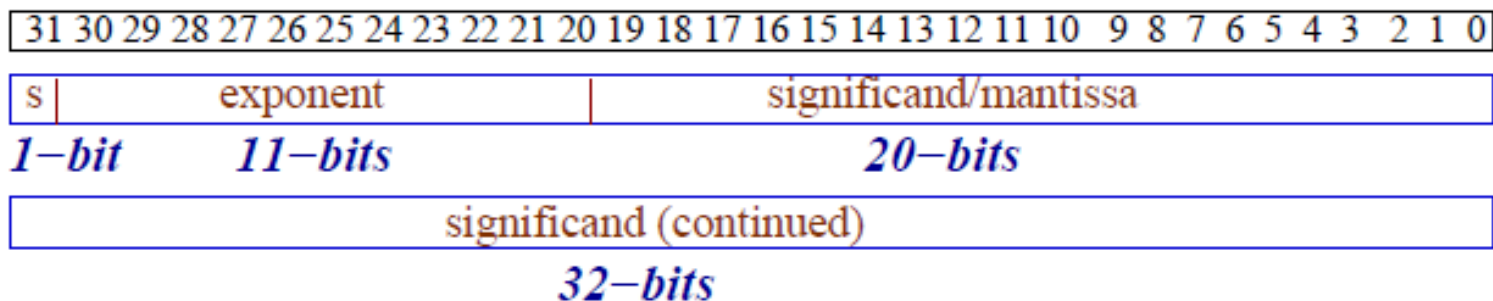

Double Precession (64-bit)

Interpretation of Bits

- The most significant bit indicates the sign of the number - one is negative and zero is positive.
- The next eight bits (11 in case of double precession) store the value of the signed exponent of two ($2^{\text{biasedExp}}$).
- Remaining 23 bits (52 in case of double precession) are for the significand (mantissa).

Types of Data

- Data represented in this format are classified in five groups.
- Normalized numbers,
- Zeros,
- Subnormal(denormal) numbers,
- Infinity and not-a-number (nan).

Single Precision Data: Interpretation

Single Precision		Data Type
<i>Exponent</i>	<i>Significand</i>	
0	0	± 0
0	nonzero	\pm subnormal number
1 - 254	anything	\pm normalized number
255	0	$\pm \infty$
255	nonzero	<i>NaN</i> (not a number)

Double Precision Data

Double Precision		Data Type
<i>Exponent</i>	<i>Significand</i>	
0	0	± 0
0	nonzero	\pm subnormal number
1 - 2046	anything	\pm normalized number
2047	0	$\pm \infty$
2047	nonzero	<i>NaN</i> (not a number)

Single Precision Normalized Number

- Let the sign bit (31) be s , the exponent (30-23)

be e and the mantissa (significand or fraction) (22-0) be m .

The valid range of the exponents is 1 to 254 (if e is treated as an unsigned number).

- The actual exponent is biased by 127
- To get e i.e. the actual value of the exponent is $e - 127$.
- This gives the range: $2^{1-127} = 2^{-126}$ to $2^{254-127} = 2^{127}$.

Single Precision Normalized Number

- The normalized significand is 1.m (binary dot).

The binary point is before bit-22 and the 1 (one) is not present explicitly.

- The sign bit $s = 1$ for a -ve number is zero (0) for a +ve number.
- The value of a normalized number is

$$(-1)^s \times 1.m \times 2^{e-127}$$

An Example

Consider the following 32-bit pattern

1 1011 0110 011 0000 0000 0000 0000

The value is

$$\begin{aligned} & (-1)^1 \times 2^{10110110-01111111} \times 1.011 \\ &= -1.375 \times 2^{55} \\ &= -49539595901075456.0 \\ &= -4.9539595901075456 \times 10^{16} \end{aligned}$$

An Example

Consider the decimal number: $+105.625$. The equivalent binary representation is

$$\begin{aligned} & +1101001.101 \\ = & +1.101001101 \times 2^6 \\ = & +1.101001101 \times 2^{133-127} \\ = & +1.101001101 \times 2^{10000101-01111111} \end{aligned}$$

In IEEE 754 format:

0 1000 0101 101 0011 0100 0000 0000 0000

An Example

Consider the decimal number: $+2.7$. The equivalent binary representation is

$$\begin{aligned} & +10.10\ 1100\ 1100\ 1100 \dots \\ = & +1.010\ 1100\ 1100 \dots \times 2^1 \\ = & +1.010\ 1100\ 1100 \dots \times 2^{128-127} \\ = & +1.010\ 1100 \dots \times 2^{10000000-01111111} \end{aligned}$$

In IEEE 754 format (approximate):

0 1000 0000 010 1100 1100 1100 1100 1101

e		Actual Exponent
0000 0000		Reserved
0000 0001	$1-127 = -126$	-126_{10}
0000 0010	$2-127 = -125$	-125_{10}
...		...
0111 1111		0_{10}
...		...
1111 1110	$254-127=127$	127_{10}
1111 1111		Reserved

E	F	meaning	Notes
00000000	0...0	0	+0.0 and -0.0
00000000	X...X	Valid number	Unnormalized $= (-1)^S \times 2^{-126} \times (0.F)$
11111111	0...0	Infinity	
11111111	X...X	Not a Number	

E	Real Exponent	F	Value
0000 0000	Reserved	000...0	0_{10}
		xxx...x	Unnormalized $(-1)^S \times 2^{-126} \times (0.F)$
0000 0001	-126_{10}		Normalized $(-1)^S \times 2^{e-127} \times (1.F)$
0000 0010	-125_{10}		
...	...		
0111 1111	0_{10}		
...	...		
1111 1110	127_{10}		
1111 1111	Reserved	000...0	Infinity
		xxx...x	NaN

Range of numbers

□ Normalized (positive range; negative is symmetric)

smallest

00000000	10000000000000000000000000000000
----------	----------------------------------

 $+2^{-126}(1+0) = 2^{-126}$

largest

01111110	11111111111111111111111111111111
----------	----------------------------------

 $+2^{127}(2-2^{-23})$

□ Unnormalized

smallest

00000000	00000000000000000000000000000001
----------	----------------------------------

 $+2^{-126}(2^{-23}) = 2^{-149}$

largest

00000000	11111111111111111111111111111111
----------	----------------------------------

 $+2^{-126}(1-2^{-23})$




-
- The smallest magnitude of a normalized number in single precession is
 - $\pm 0000\ 0001\ 000\ 0000\ 0000\ 0000\ 0000\ 0000$, whose value is 1.0×2^{-126} .
 - The largest magnitude of a normalized number in single precession is
 - $\pm 1111\ 1110\ 111\ 1111\ 1111\ 1111\ 1111\ 1111$, whose value is
 - $1.999999988 \times 2^{127} \approx 3.403 \times 10^{38}$

-
- The smallest magnitude of a **subnormal** number in single precision is $\pm 0000\ 0000\ 000\ 0000\ 0000\ 0000\ 0000\ 0001$, whose value is $2^{-126+(-23)} = 2^{-149}$.
 - The largest magnitude of a **subnormal** number in single precision is $\pm 0000\ 0000\ 111\ 1111\ 1111\ 1111\ 1111\ 1111$, whose value is $0.99999988 \times 2^{-126}$.


-
- The smallest subnormal 2^{-149} is closer to zero.
 - The largest subnormal $0.999999988 \times 2^{-126}$ is closer to the smallest normalized number 1.0×2^{-126} .

-
- ❑ There *aren't* more **IEEE** numbers.
 - ❑ With 32 bits, there are 2^{32} , or about 4 billion, different bit patterns.
 - These can represent 4 billion integers *or* 4 billion reals.
 - But there are an infinite number of reals, and the **IEEE** format can only represent *some* of the ones from about -2^{128} to $+2^{128}$.
 - Represent same number of values between 2^n and 2^{n+1} as 2^{n+1} and 2^{n+2}

 


- ❑ Thus, floating-point arithmetic has “issues”
 - Small roundoff errors can accumulate with multiplications or exponentiations, resulting in big errors.
 - Rounding errors can invalidate many basic arithmetic principles such as the associative law, $(x + y) + z = x + (y + z)$.
- ❑ The **IEEE 754** standard guarantees that all machines will produce the same results—but those results may not be mathematically accurate!

Expressible Numbers

 


(a) Two's Complement Integers

 

(b) Floating-Point Numbers

Density of Floating Point Numbers

 

Arithmetic

Addition/subtraction of signed numbers

x_i	y_i	Carry-in c_i	Sum s_i	Carry-out c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

At the i^{th} stage:

Input:

c_i is the carry-in

Output:


s_i is the sum

c_{i+1} carry-out to $(i+1)^{st}$ state


$$s_i = \overline{x_i}y_i\overline{c_i} + \overline{x_i}y_ic_i + x_i\overline{y_i}\overline{c_i} + x_iy_ic_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = y_ic_i + x_ic_i + x_iy_i$$

Example:

 

Addition logic for a single stage

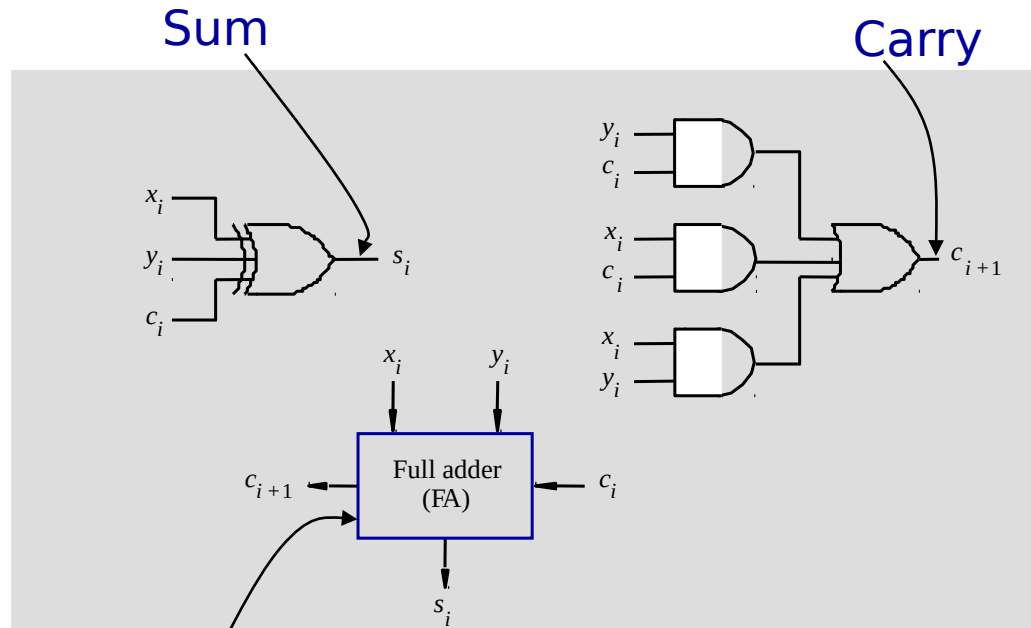


Full Adder (FA): Symbol for the complete circuit for a single stage of addition.

n -bit adder

Cascade n full adder (FA) blocks to form a n -bit adder.

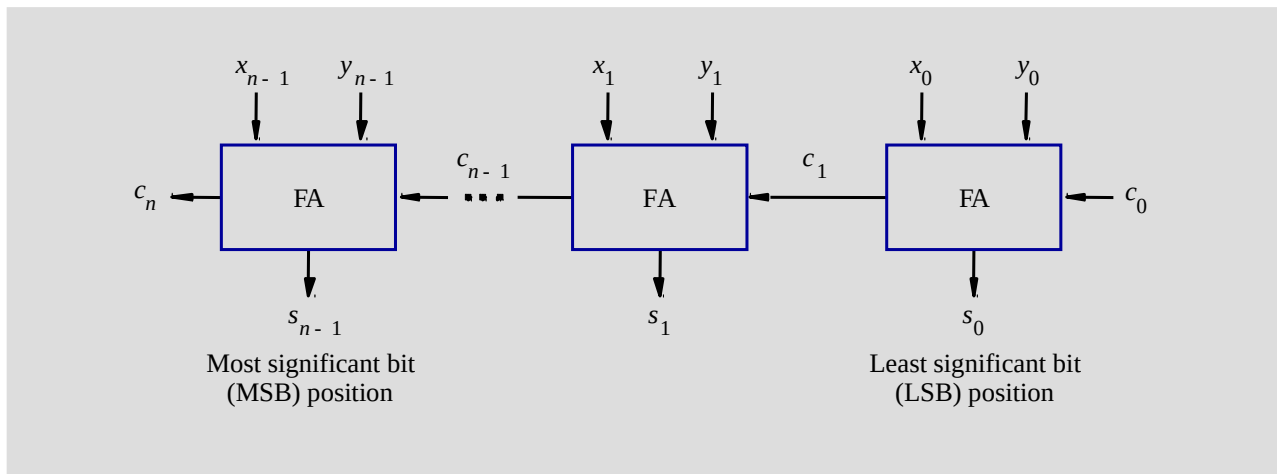
Carries propagate or ripple through this cascade, n -bit ripple carry adder.



Carry-in c_0 into the LSB position provides a convenient way to perform subtraction.

K n -bit adder

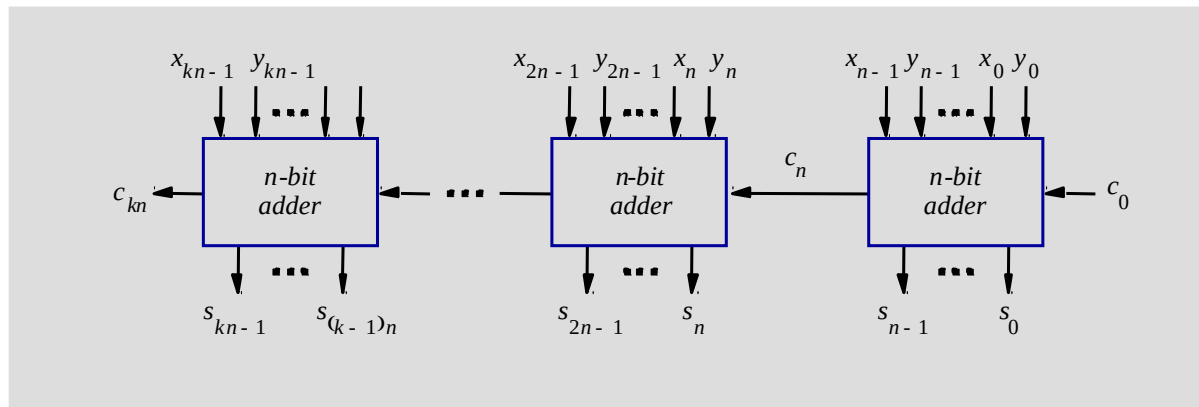
K n -bit numbers can be added by cascading k n -bit adders.




Each n -bit adder forms a block, so this is cascading of blocks.
Carries ripple or propagate through blocks, [Blocked Ripple Carry Adder](#)

n -bit subtractor

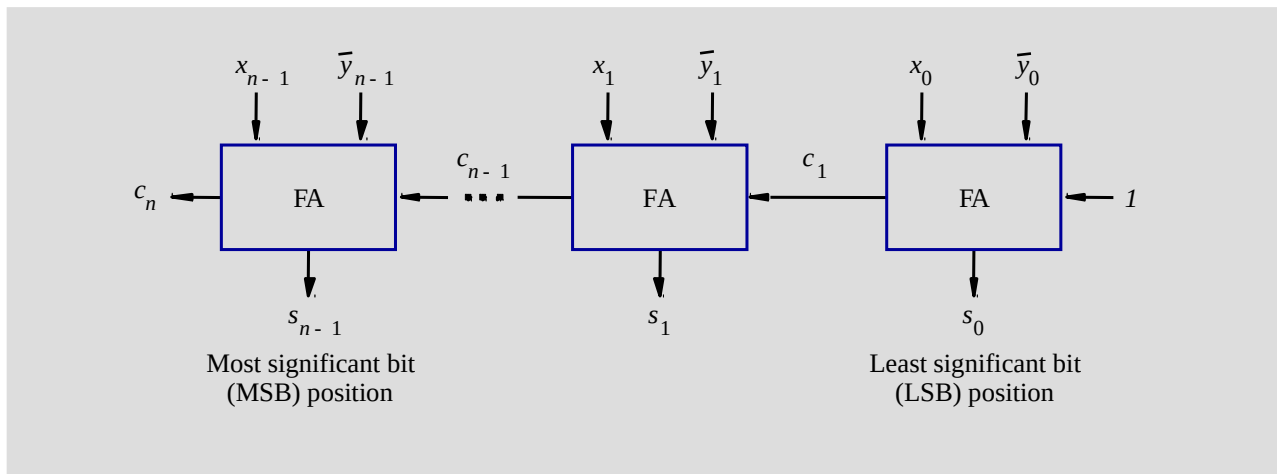- Recall $X - Y$ is equivalent to adding 2's complement of Y to X .
- 2's complement is equivalent to 1's complement + 1.
- $X - Y = X + Y + 1$
- 2's complement of positive and negative numbers is computed similarly.



n -bit adder/subtractor (contd..)

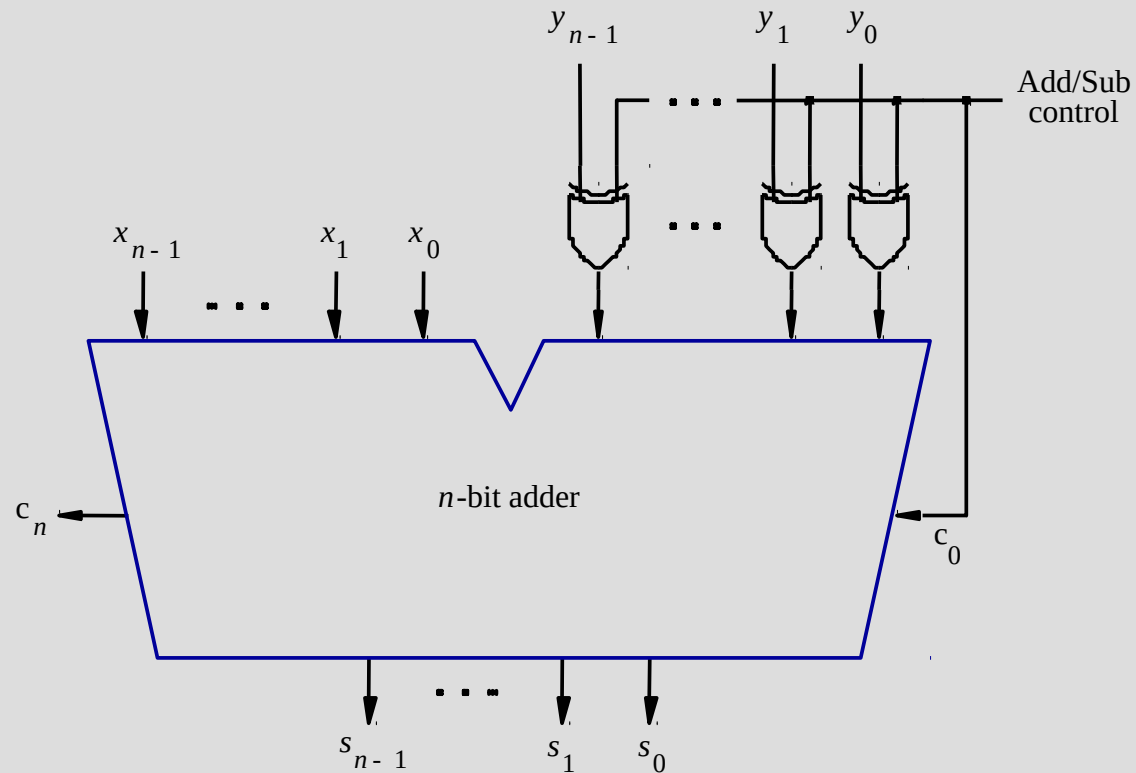

- Add/sub control = 0, addition.
- Add/sub control = 1, subtraction.

Detecting overflows

Overflows can only occur when the sign of the two operands is the same.

Overflow occurs if the sign of the result is different from the sign of the operands.

Recall that the MSB represents the sign.


- x_{n-1} , y_{n-1} , s_{n-1} represent the sign of operand x , operand y and result s respectively.

Circuit to detect overflow can be implemented by the following logic expressions:

$$\text{Overflow} = x_{n-1}y_{n-1}\bar{s}_{n-1} + \bar{x}_{n-1}\bar{y}_{n-1}s_{n-1}$$


$$\text{Overflow} = c_n \oplus c_{n-1}$$

Computing the add time

 


Consider 0^{th} stage:

 - c_1 is available after 2 gate delays.
- s_1 is available after 1 gate delay.



Computing the add time (contd..)

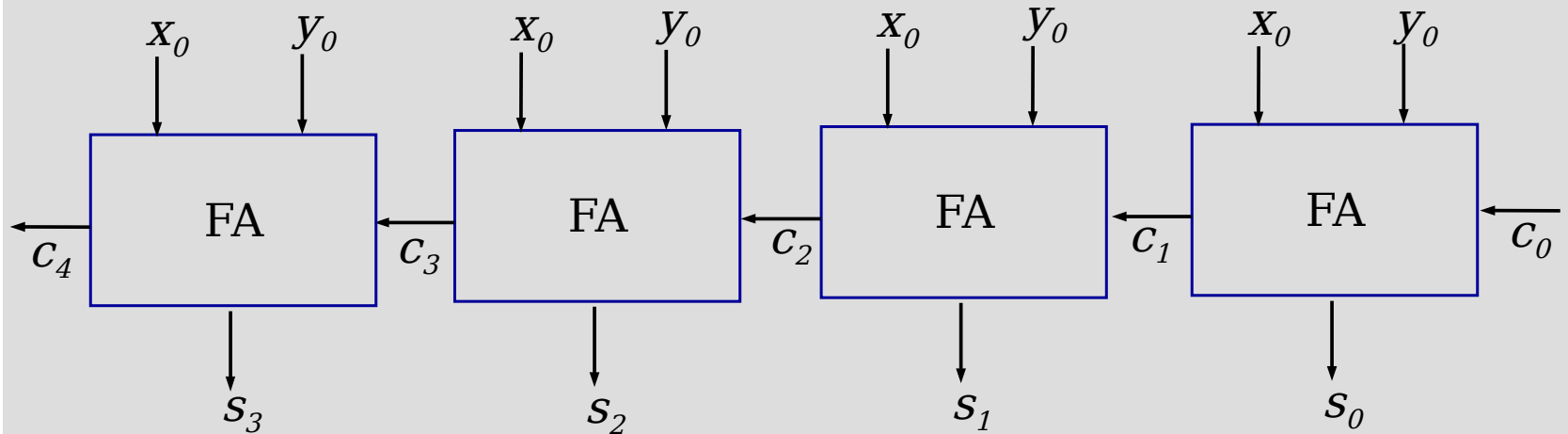Cascade of 4 Full Adders, or a 4-bit adder



- s_0 available after 1 gate delays, c_1 available after 2 gate delays.
- s_1 available after 3 gate delays, c_2 available after 4 gate delays.
- s_2 available after 5 gate delays, c_3 available after 6 gate delays.
- s_3 available after 7 gate delays, c_4 available after 8 gate delays.

For an n -bit adder, s_{n-1} is available after $2n-1$ gate delays
 c_n is available after $2n$ gate delays.

Fast addition

Recall the equations:

$$s_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Second equation can be written as:

$$c_{i+1} = x_i y_i + (x_i + y_i) c_i$$

We can write:

$$c_{i+1} = G_i + P_i c_i$$

$$\text{where } G_i = x_i y_i \text{ and } P_i = x_i + y_i$$

- G_i is called generate function and P_i is called propagate function
- G_i and P_i are computed only from x_i and y_i and not c_i , thus they can be computed in one gate delay after X and Y are applied to the inputs of an n -bit adder.

Carry lookahead

$$c_{i+1} = G_i + P_i c_i$$

$$c_i = G_{i-1} + P_{i-1} c_{i-1}$$

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} c_{i-1})$$

continuing

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} c_{i-2}))$$

until

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$


- All carries can be obtained 3 gate delays after X , Y and c_0 are applied.

- One gate delay for P_i and G_i


- Two gate delays in the AND-OR circuit for c_{i+1}

- All sums can be obtained 1 gate delay after the carries are computed.
- Independent of n , n -bit addition requires only 4 gate delays.
- This is called Carry Lookahead adder.

Carry-lookahead adder

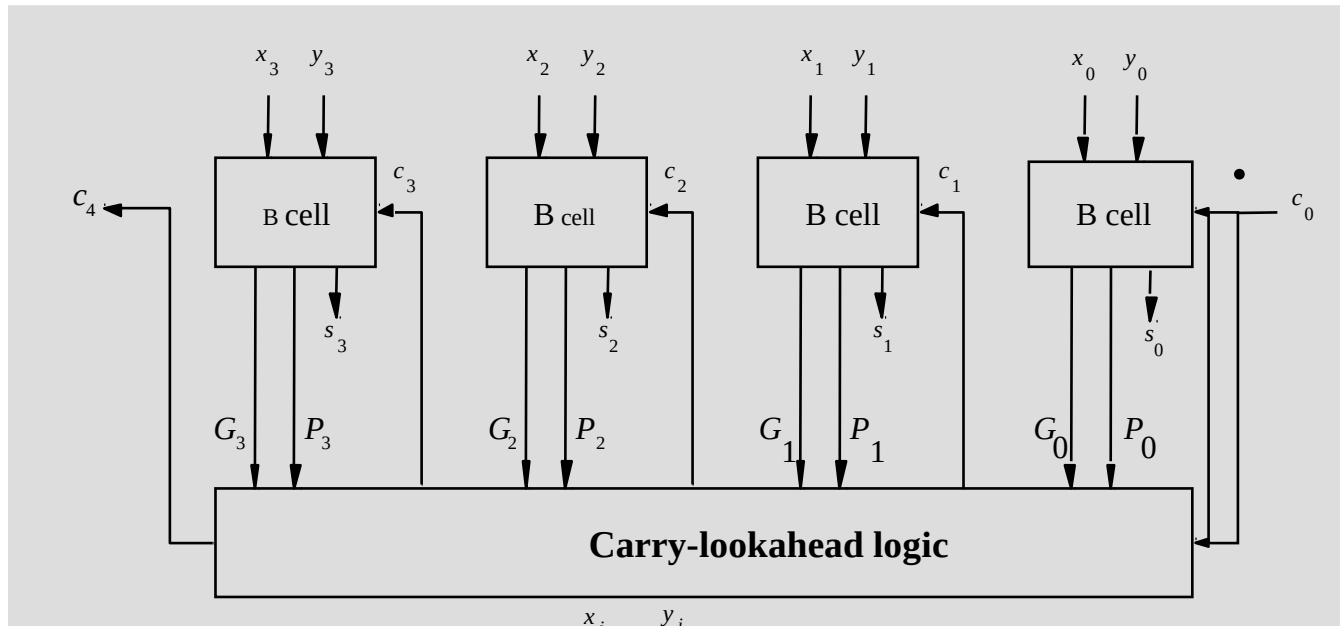

**4-bit
carry-lookahead
adder**

 

B-cell for a single stage

Carry lookahead adder (contd..)


Performing n -bit addition in 4 gate delays independent of n is good only theoretically because of fan-in constraints.

Last, and gate and carry gate require a fan-in of $(P_i G_i + P_i P_{i-1} G_{i-1} + P_i P_{i-1} P_{i-2} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0)$ for a n -bit adder.

- For a 4-bit adder ($n=4$) fan-in of 5 is required.
- Practical limit for most gates.

In order to add operands longer than 4 bits, we can cascade 4-bit Carry-Lookahead adders. Cascade of Carry-Lookahead adders is called Blocked Carry-Lookahead adder.

4-bit carry-lookahead Adder

 

~~Blocked Carry-Lookahead adder~~

Carry-out from a 4-bit block can be given as:

$$c_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

Rewrite this as:

$$P_0^I = P_3 P_2 P_1 P_0$$


$$G_0^I = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$

Subscript I denotes the blocked carry lookahead and identifies the block.

Cascade 4 4-bit adders, c_{16} can be expressed as:

$$c_{16} = G_3^I + P_3^I G_2^I + P_3^I P_2^I G_1^I + P_3^I P_2^I P_1^0 G_0^I + P_3^I P_2^I P_1^0 P_0^0 c_0$$

Blocked Carry-Lookahead adder

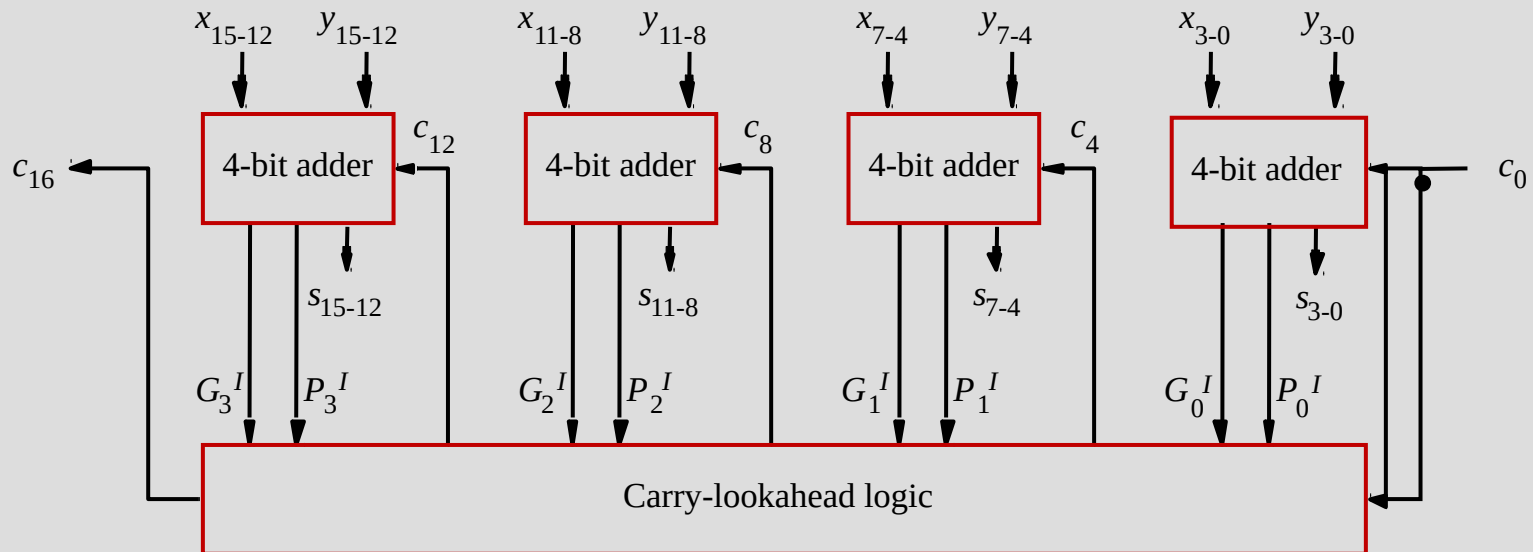

After x_i, y_i and c_0 are applied as inputs:

- G_i and P_i for each stage are available after 1 gate delay.
- P^I is available after 2 and G^I after 3 gate delays.
- All carries are available after 5 gate delays.
- c_{16} is available after 5 gate delays.
- s_{15} which depends on c_{12} is available after 8 (5+3) gate delays
(Recall that for a 4-bit carry lookahead adder, the last sum bit is available 3 gate delays after all inputs are available)

Multiplication

~~Multiplication of unsigned numbers~~

1	1	0	1	(13) Multiplicand M
1	0	1	1	(11) Multiplier Q
<hr/>				
1	1	0	1	
1	1	0	1	
0	0	0	0	
1	1	0	1	
<hr/>				
1	0	0	0	1
0	1	1	1	1
1	1	1	1	1
1	0	0	0	1
<hr/>				
1	0	0	0	1
0	1	1	1	1
1	1	1	1	1
1	0	0	0	1
<hr/>				
1	0	0	0	1
0	1	1	1	1
1	1	1	1	1
1	0	0	0	1
<hr/>				
1	0	0	0	1
0	1	1	1	1
1	1	1	1	1
1	0	0	0	1
<hr/>				
1	0	0	0	1
0	1	1	1	1

Product of 2 n -bit numbers is at most a $2n$ -bit number.

Unsigned multiplication can be viewed as addition of shifted versions of the multiplicand.

~~Multiplication of unsigned numbers~~ (contd..)

We added the partial products at end.


- Alternative would be to add the partial products at each stage.

Rules to implement multiplication are:

- If the j^{th} bit of the multiplier is 1, shift the multiplicand and add the shifted multiplicand to the current value of the partial product.
- Hand over the partial product to the next stage
- Value of the partial product at the start stage is 0.


Multiplication of unsigned numbers

Typical multiplication cell

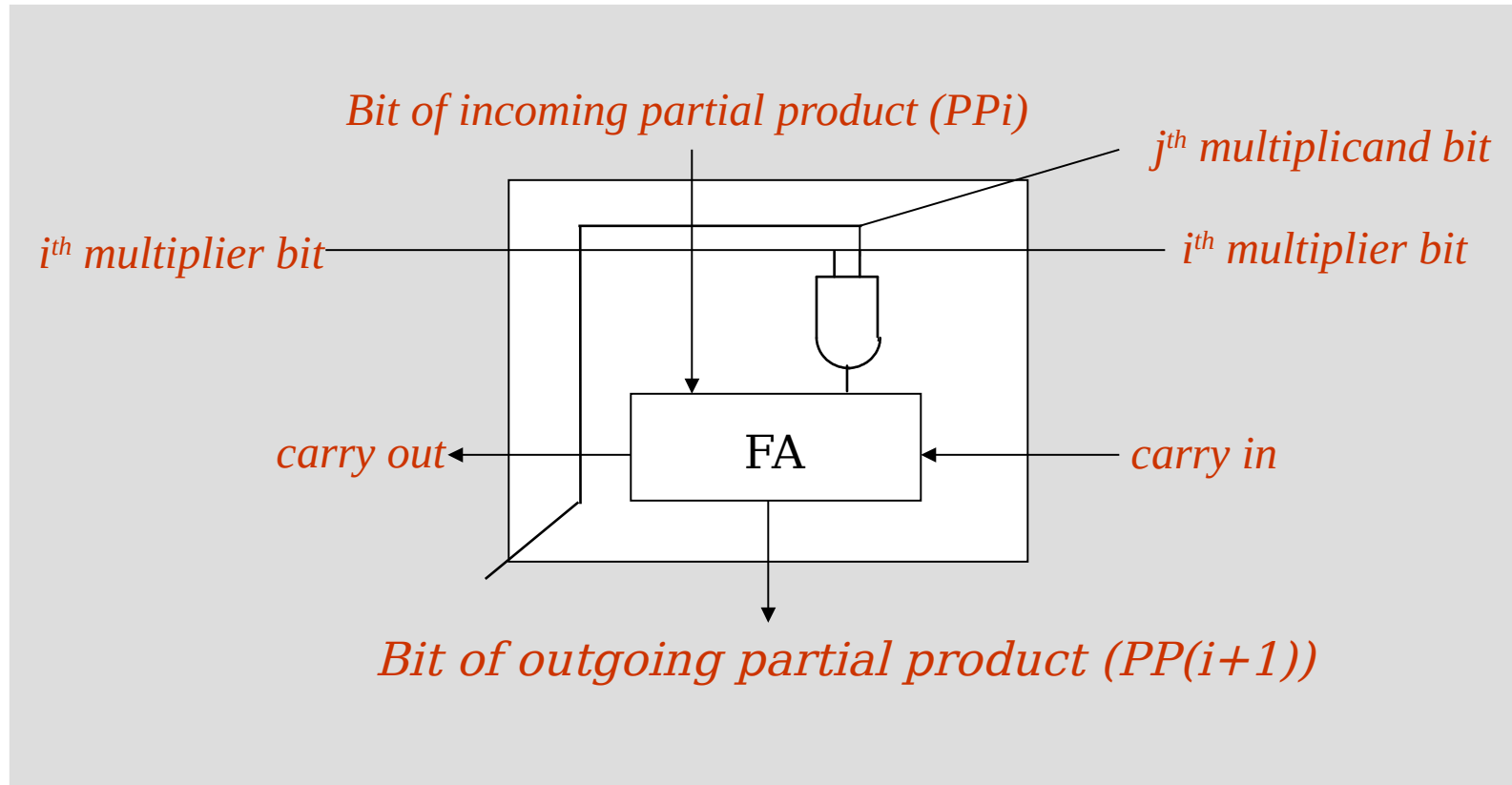

Combinatorial array multiplier

Combinatorial array multiplier

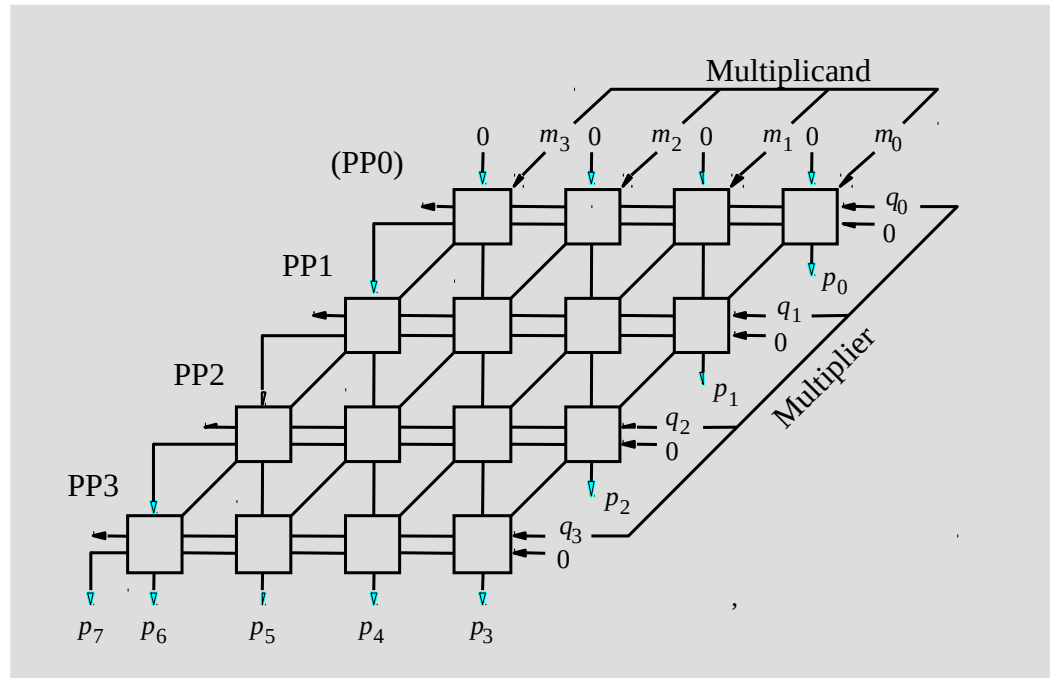

Product is: p_7, p_6, \dots, p_0

Multiplicand is shifted by displacing it through an array of adders.


Combinatorial array multiplier (contd..)

- Combinatorial array multipliers are:
 - Extremely inefficient.
 - Have a high gate count for multiplying numbers of practical size such as 32-bit or 64-bit numbers.
 - Perform only one function, namely, unsigned integer product.
- Improve gate efficiency by using a mixture of combinatorial array techniques and sequential techniques requiring less combinational logic.


Sequential multiplication

- Recall the rule for generating partial products:
 - If the i th bit of the multiplier is 1, add the appropriately shifted multiplicand to the current partial product.
 - Multiplicand has been shifted left when added to the partial product.
- However, adding a left-shifted multiplicand to an unshifted partial product is equivalent to adding an unshifted multiplicand to a right-shifted partial product.


Sequential Circuit Multiplier

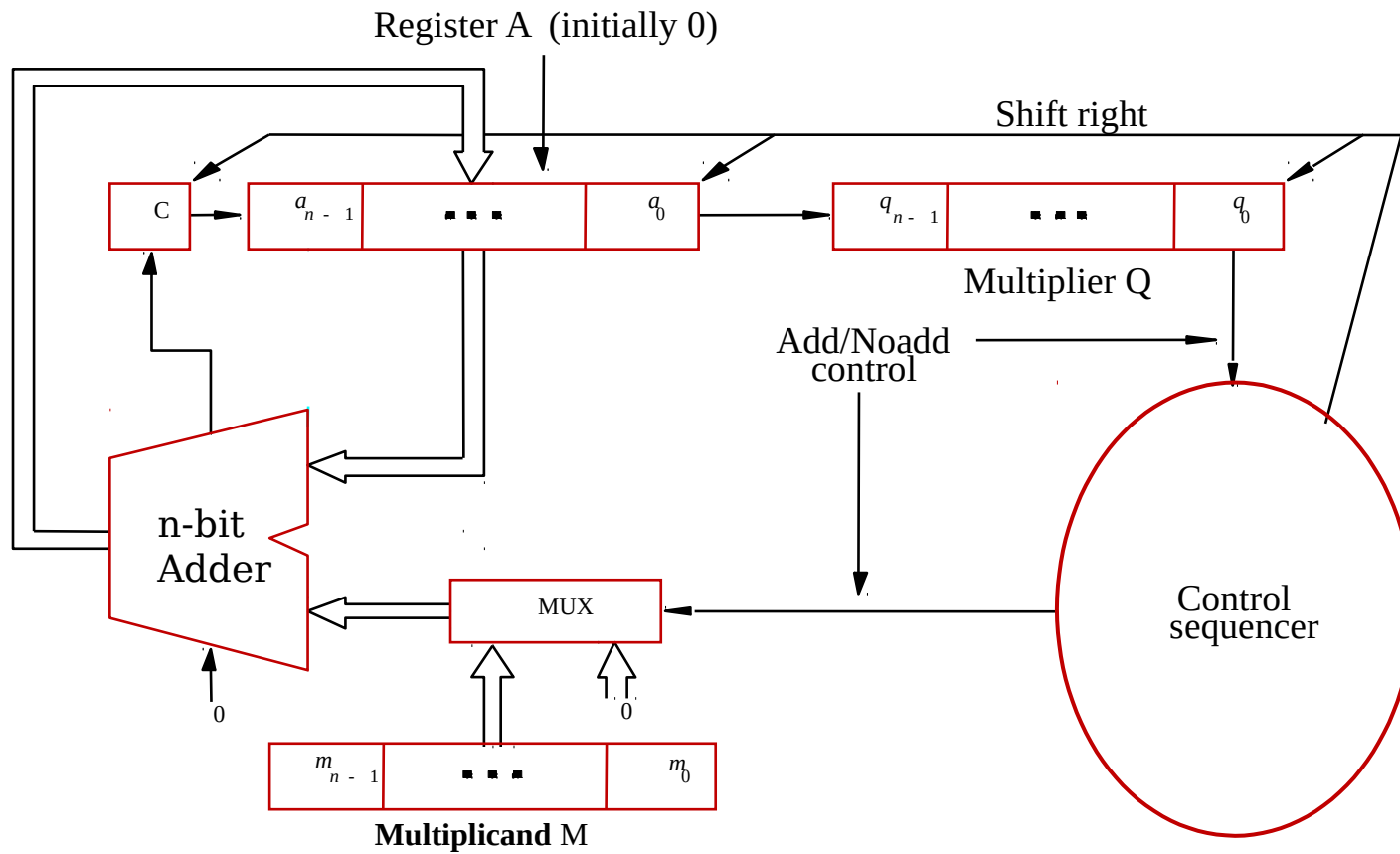

Sequential multiplication (contd..)

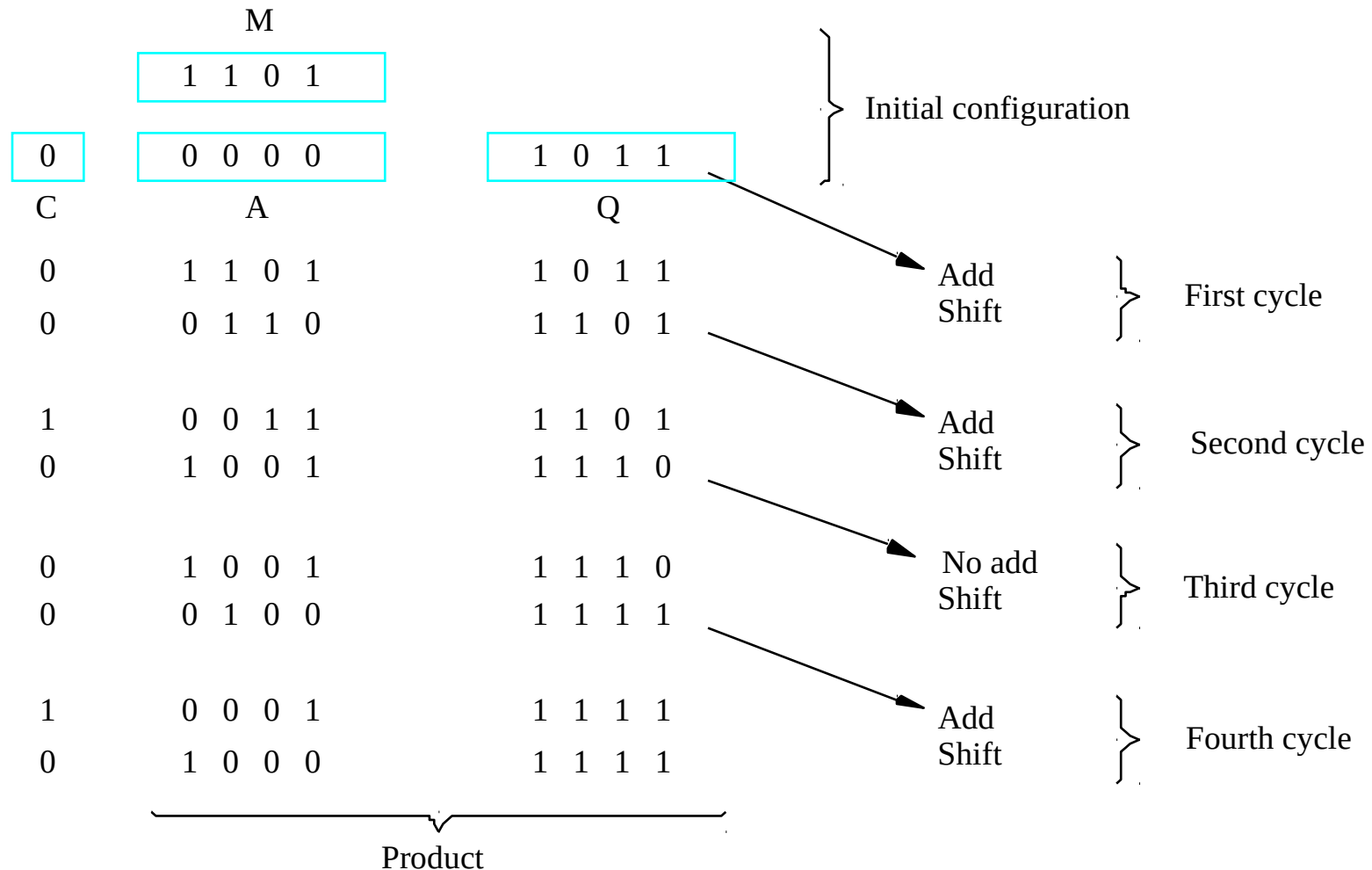


Unsigned Binary Multiplication

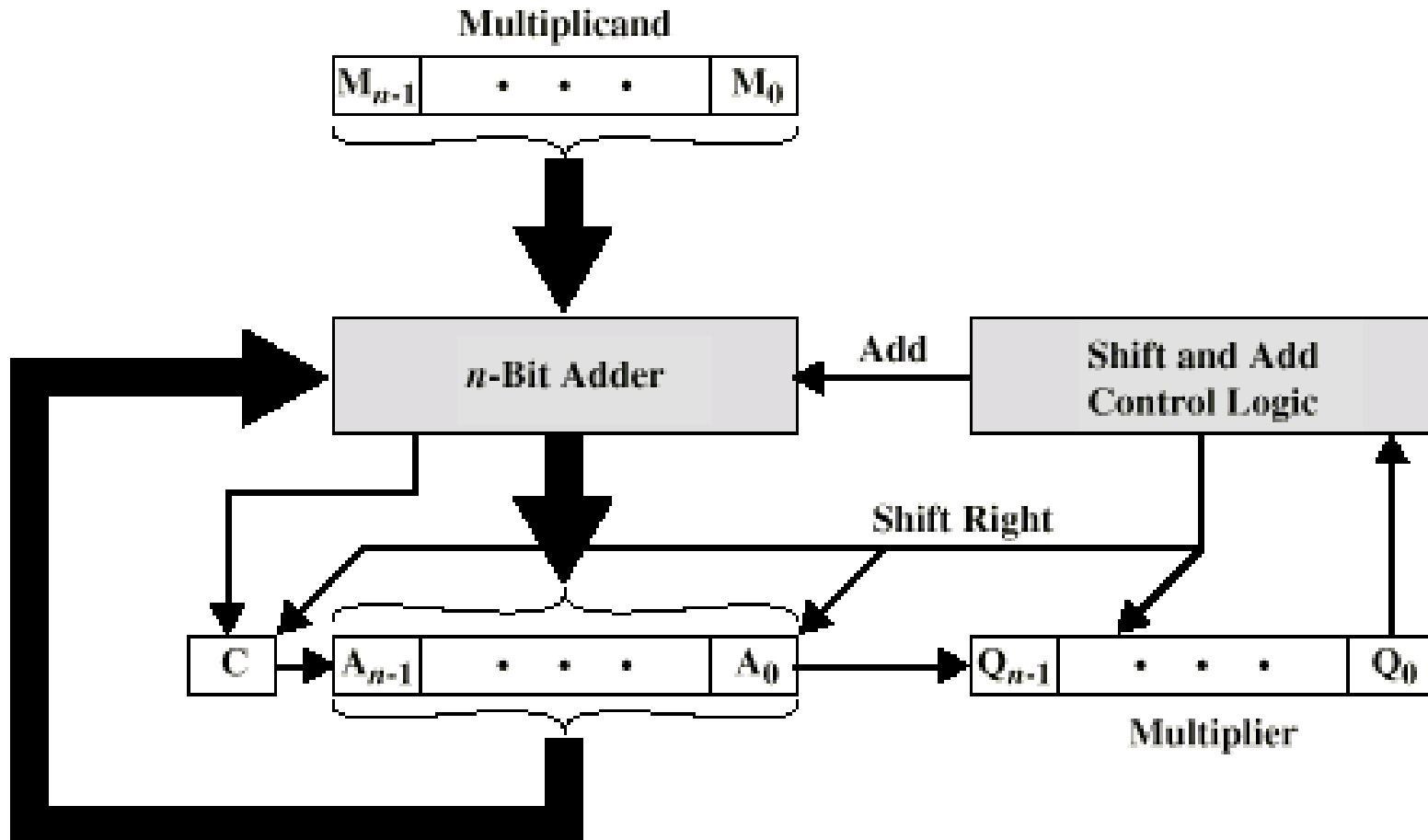

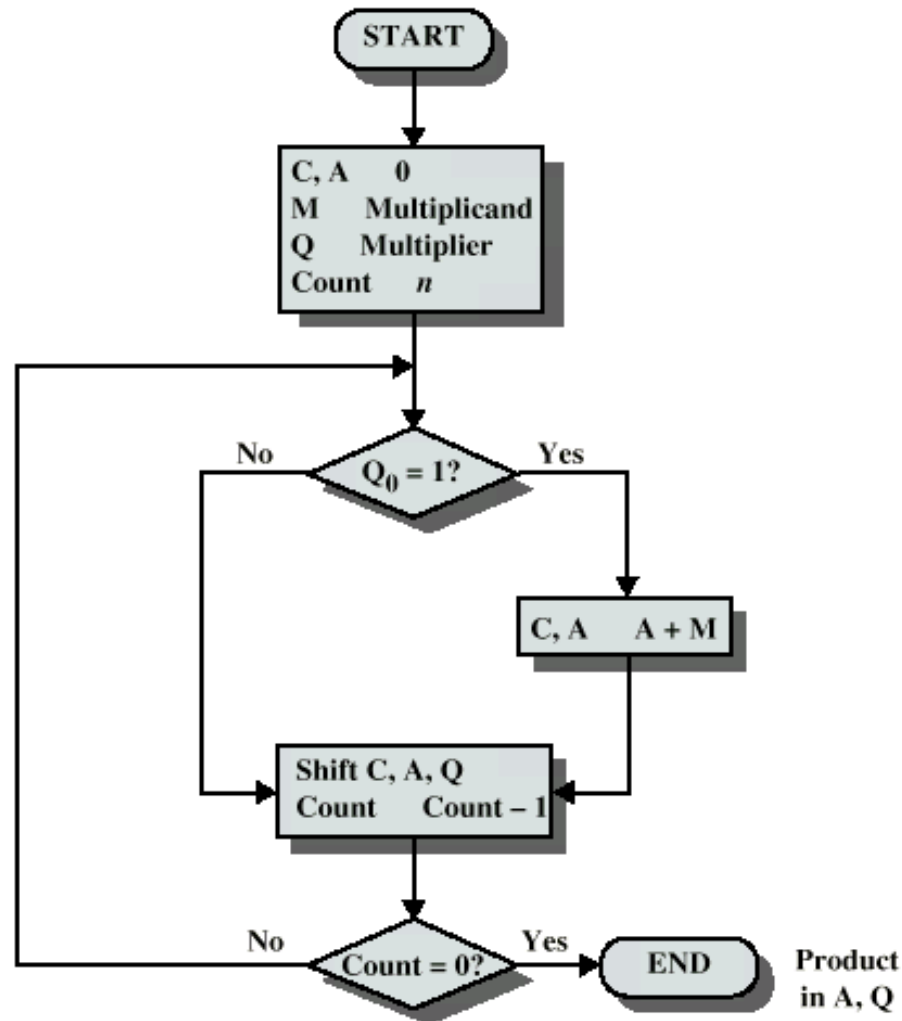(a) Block Diagram

Flowchart for Unsigned Binary Multiplication



Execution of Example

C	A	Q	M		
0	0000	1101	1011	Initial Values	
0	1011	1101	1011	Add	} First Cycle
0	0101	1110	1011	Shift	
0	0010	1111	1011	Shift	} Second Cycle
0	1101	1111	1011	Add	
0	0110	1111	1011	Shift	} Third Cycle
1	0001	1111	1011	Add	
0	1000	1111	1011	Shift	} Fourth Cycle

Signed Multiplication

Signed Multiplication

- Considering 2's-complement signed operands, what will happen to $(-13) \times (+11)$ if following the same method of unsigned multiplication?

Sign extension is shown in blue

					1	0	0	1	1	(- 13)
					0	1	0	1	1	(+ 11)
					<hr/>					
	1	1	1	1	1	0	0	1	1	
	1	1	1	1	1	0	0	1	1	
	0	0	0	0	0	0	0	0		
	1	1	1	0	0	1	1			
	0	0	0	0	0	0				
	<hr/>									
	1	1	0	1	1	1	0	0	0	1 (- 143)

Sign extension of negative multiplicand.

Signed Multiplication

- For a negative multiplier, a straightforward solution is to form the 2's-complement of both the multiplier and the multiplicand and proceed as in the case of a positive multiplier.
- This is possible because complementation of both operands does not change the value or the sign of the product.
- A technique that works equally well for both negative and positive multipliers – Booth algorithm.

Booth Algorithm

- Consider in a multiplication, the multiplier is positive 0011110, how many appropriately shifted versions of the multiplicand are added in a standard procedure?

$$\begin{array}{r}
 \begin{array}{ccccccc}
 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 0 & 0 & +1 & +1 & +1 & +1 & 0 \\
 \hline
 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 \hline
 0 & 0 & 0 & 1 & 0 & 1 & 0 & 1 & 0 & 0 & 0 & 1 & 1 & 0
 \end{array}
 \end{array}$$


Booth Algorithm

- Since $0011110 = 0100000 - 0000010$, if we use the expression to the right, what will happen?

								0	1	0	1	1	0	1		
								0	+	1	0	0	0	-	1	0
								<hr/>								
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	
1	1	1	1	1	1	1	1	0	1	0	0	1	1	←		2's complement of the multiplicand
0	0	0	0	0	0	0	0	0	0	0	0	0	0			
0	0	0	0	0	0	0	0	0	0	0	0					
0	0	0	0	0	0	0	0	0	0	0						
0	0	0	1	0	1	1	0	1								
0	0	0	0	0	0	0	0	0								
<hr/>								0	0	0	1	0	1	0		

Booth Algorithm

- In general, in the Booth scheme, -1 times the shifted multiplicand is selected when moving from 0 to 1, and +1 times the shifted multiplicand is selected when moving from 1 to 0, as the multiplier is scanned from right to left.

0	0	1	0	1	1	0	0	1	1	1	0	1	0	1	1	0	0
																	
0	+1	-1	+1	0	-1	0	+1	0	0	-1	+1	-1	+1	0	-1	0	0

Booth recoding of a multiplier.

Booth Algorithm

$\begin{array}{r} 01101 \quad (+13) \\ \times 11010 \quad (-6) \\ \hline \end{array}$	\Rightarrow	$\begin{array}{r} 01101 \\ 0-1+1-10 \\ \hline \end{array}$
		$\begin{array}{r} 00000 \\ 11111 \\ 00001 \\ 11100 \\ 00000 \\ \hline 1110110010 \quad (-78) \end{array}$

Booth multiplication with a negative multiplier.

Booth Algorithm


Multiplier		Version of multiplicand selected by bit i
Bit i	Bit $i-1$	
0	0	0 $\times M$
0	1	+ 1 $\times M$
1	0	- 1 $\times M$
1	1	0 $\times M$

Booth multiplier recoding table.


Booth Algorithm

- Best case – a long string of 1's (skipping over 1s)
- Worst case – 0's and 1's are alternating


Worst-case multiplier

0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
															
+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1	+1	-1


Ordinary multiplier

1	1	0	0	0	1	0	1	1	0	1	1	1	1	0	0
															
0	-1	0	0	+1	-1	+1	0	-1	+1	0	0	0	-1	0	0

Good multiplier

0	0	0	0	1	1	1	1	1	0	0	0	0	1	1	1
															
0	0	0	+1	0	0	0	0	-1	0	0	0	+1	0	0	-1

Booth's Algorithm

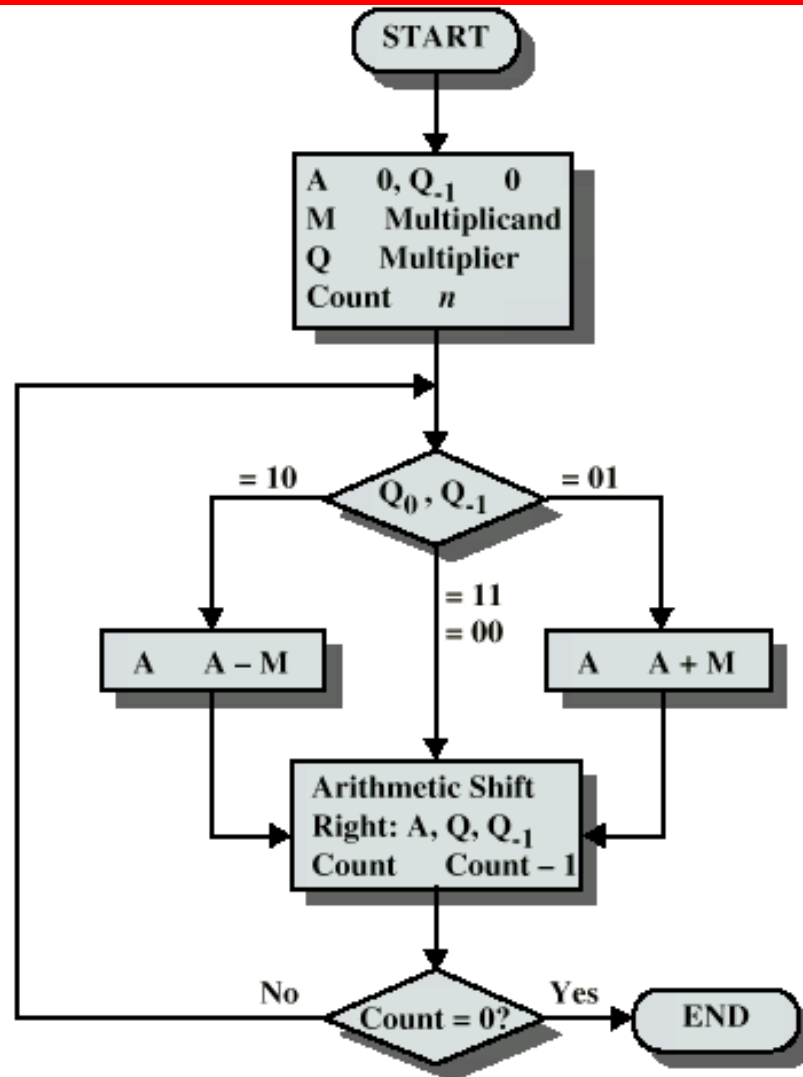


Example of Booth's Algorithm

A	Q	Q ₋₁	M	Initial Values	
0000	0011	0	0111		
1001	0011	0	0111	A A - M	} First Cycle
1100	1001	1	0111	Shift	
1110	0100	1	0111	Shift	} Second Cycle
0101	0100	1	0111	A A + M	
0010	1010	0	0111	Shift	} Third Cycle
0001	0101	0	0111	Shift	
					} Fourth Cycle

Fast Multiplication

Bit-Pair Recoding of Multipliers

 - Bit-pair recoding halves the maximum number of summands (versions of the multiplicand).



(a) Example of bit-pair recoding derived from Booth recoding

Bit-Pair Recoding of Multipliers

Multiplier bit-pair		Multiplier bit on the right $i - 1$	Multiplicand selected at position i
$i + 1$	i		
0	0	0	0 X M
0	0	1	+ 1 X M
0	1	0	+ 1 X M
0	1	1	+ 2 X M
1	0	0	- 2 X M
1	0	1	- 1 X M
1	1	0	- 1 X M
1	1	1	0 X M

(b) Table of multiplicand selection decisions

Bit-Pair Recoding of Multipliers

$$\begin{array}{r} 0\ 1\ 1\ 0\ 1\ (+13) \\ \times 1\ 1\ 0\ 1\ 0\ (-6) \\ \hline \end{array}$$



$$\begin{array}{r} 0\ 1\ 1\ 0\ 1 \\ 0\ -1\ +1\ -1\ 0 \\ \hline 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0\ 0 \\ 1\ 1\ 1\ 1\ 1\ 0\ 0\ 1\ 1 \\ 0\ 0\ 0\ 0\ 1\ 1\ 0\ 1 \\ 1\ 1\ 1\ 0\ 0\ 1\ 1 \\ 0\ 0\ 0\ 0\ 0\ 0 \\ \hline 1\ 1\ 1\ 0\ 1\ 1\ 0\ 0\ 1\ 0\ (-78) \end{array}$$




$$\begin{array}{r} 0\ 1\ 1\ 0\ 1 \\ 0\ -1\ -2 \\ \hline 1\ 1\ 1\ 1\ 1\ 0\ 0\ 1\ 1\ 0 \\ 1\ 1\ 1\ 1\ 0\ 0\ 1\ 1 \\ 0\ 0\ 0\ 0\ 0\ 0 \\ \hline 1\ 1\ 1\ 0\ 1\ 1\ 0\ 0\ 1\ 0 \end{array}$$


Figure 6.15. Multiplication requiring only $n/2$ summands.

Carry-Save Addition of Summands

- CSA speeds up the addition process.

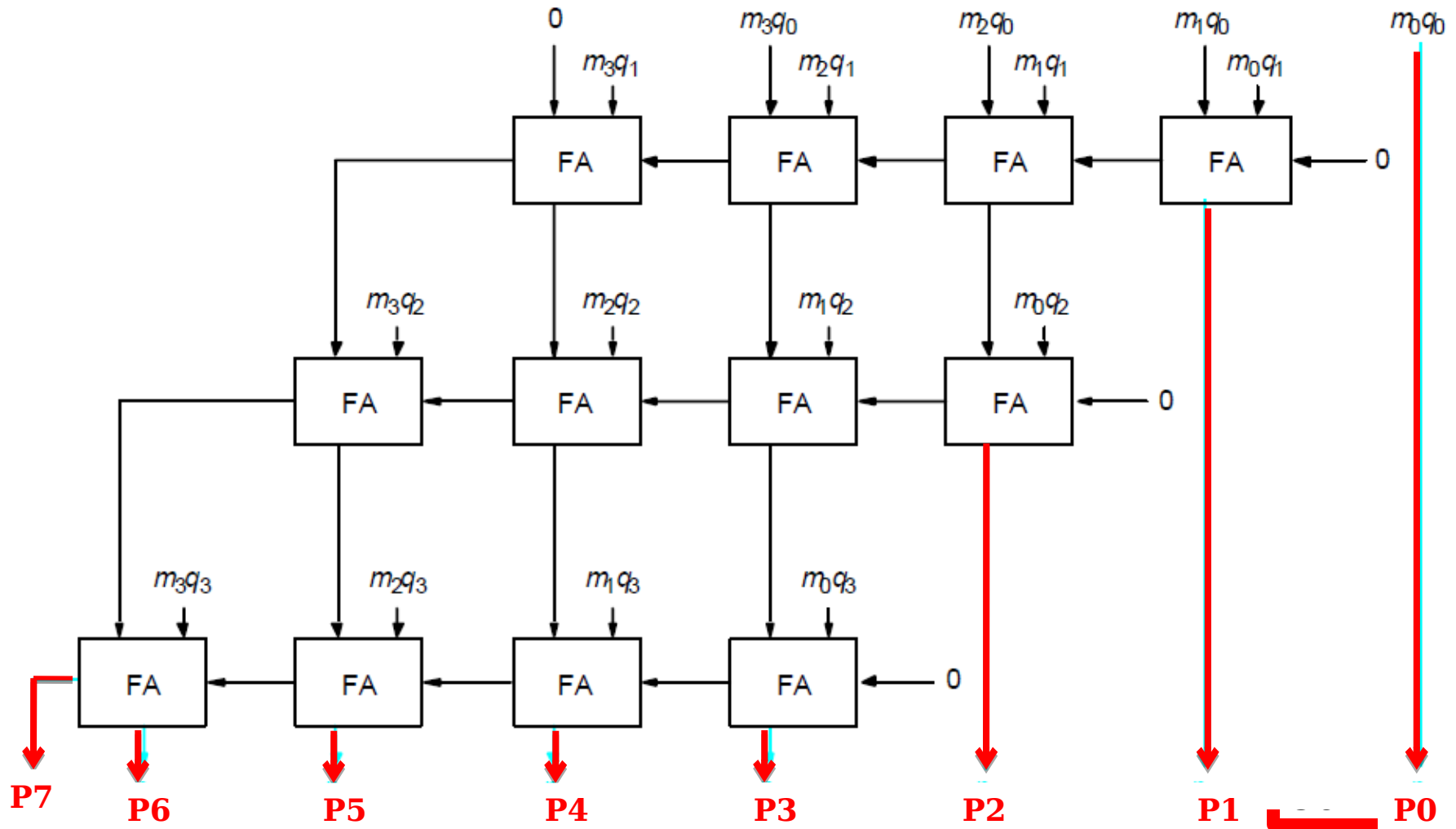

Carry-Save Addition of Summands(Cont.,)

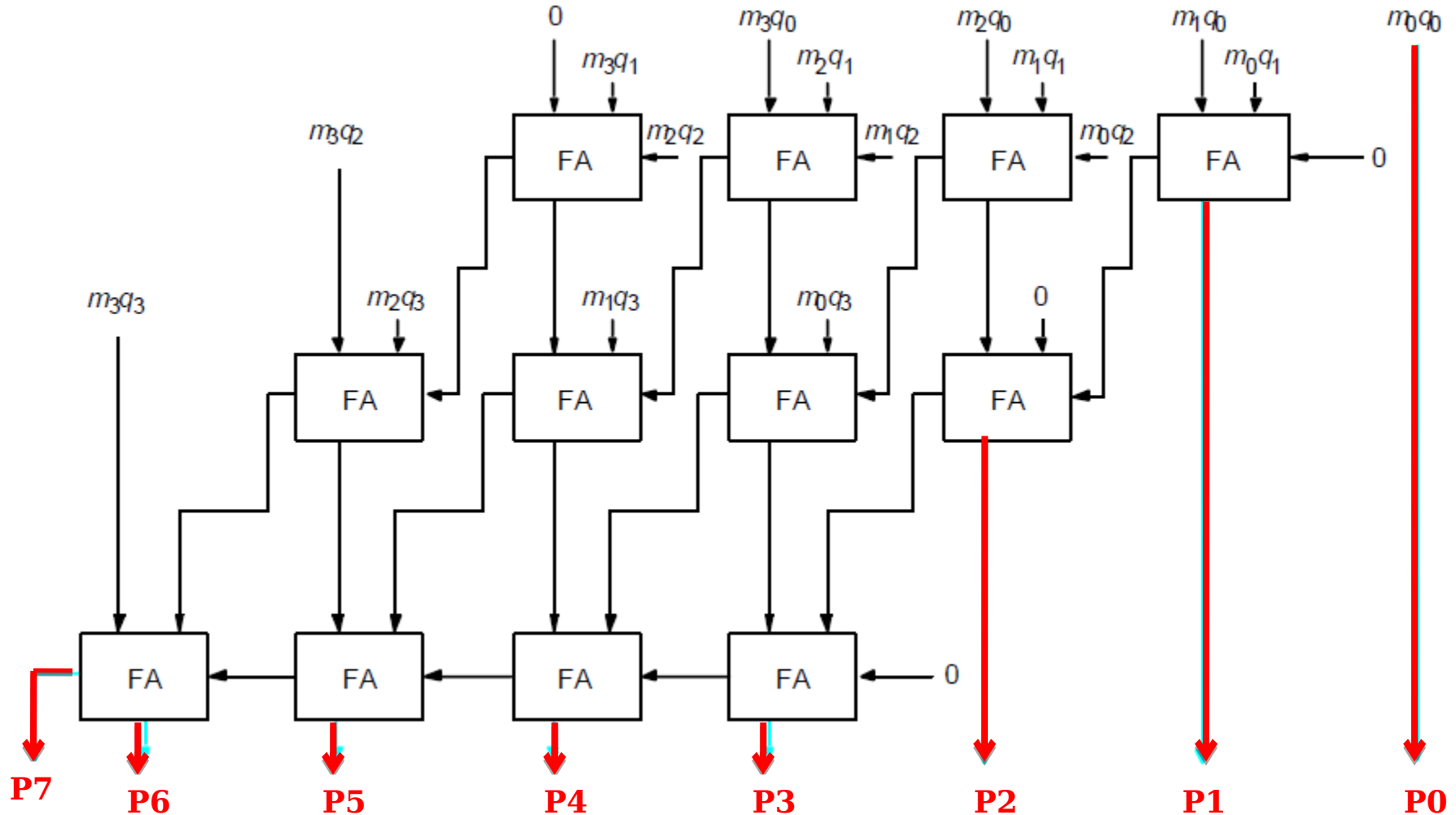

Carry-Save Addition of Summands(Cont.,)

- Consider the addition of many summands, we can:
 - Group the summands in threes and perform carry-save addition on each of these groups in parallel to generate a set of S and C vectors in one full-adder delay
 - Group all of the S and C vectors into threes, and perform carry-save addition on them, generating a further set of S and C vectors in one more full-adder delay
 - Continue with this process until there are only two vectors remaining
 - They can be added in a RCA or CLA to produce the desired product

							1	0	1	1	0	1	(45)	M
						x	1	1	1	1	1	1	(63)	Q
							1	0	1	1	0	1	A	
					1		0	1	1	0	1		B	
				1	0		1	1	0	1			C	
			1	0	1		1	0	1				D	
		1	0	1	1		0	1					E	
	1	0	1	1	0		1						F	
1	0	1	1	0	0	0	0	1	0	0	1	1	(2,835)	Product

Figure 6.17. A multiplication example used to illustrate carry-save addition as shown in Figure 6.18.

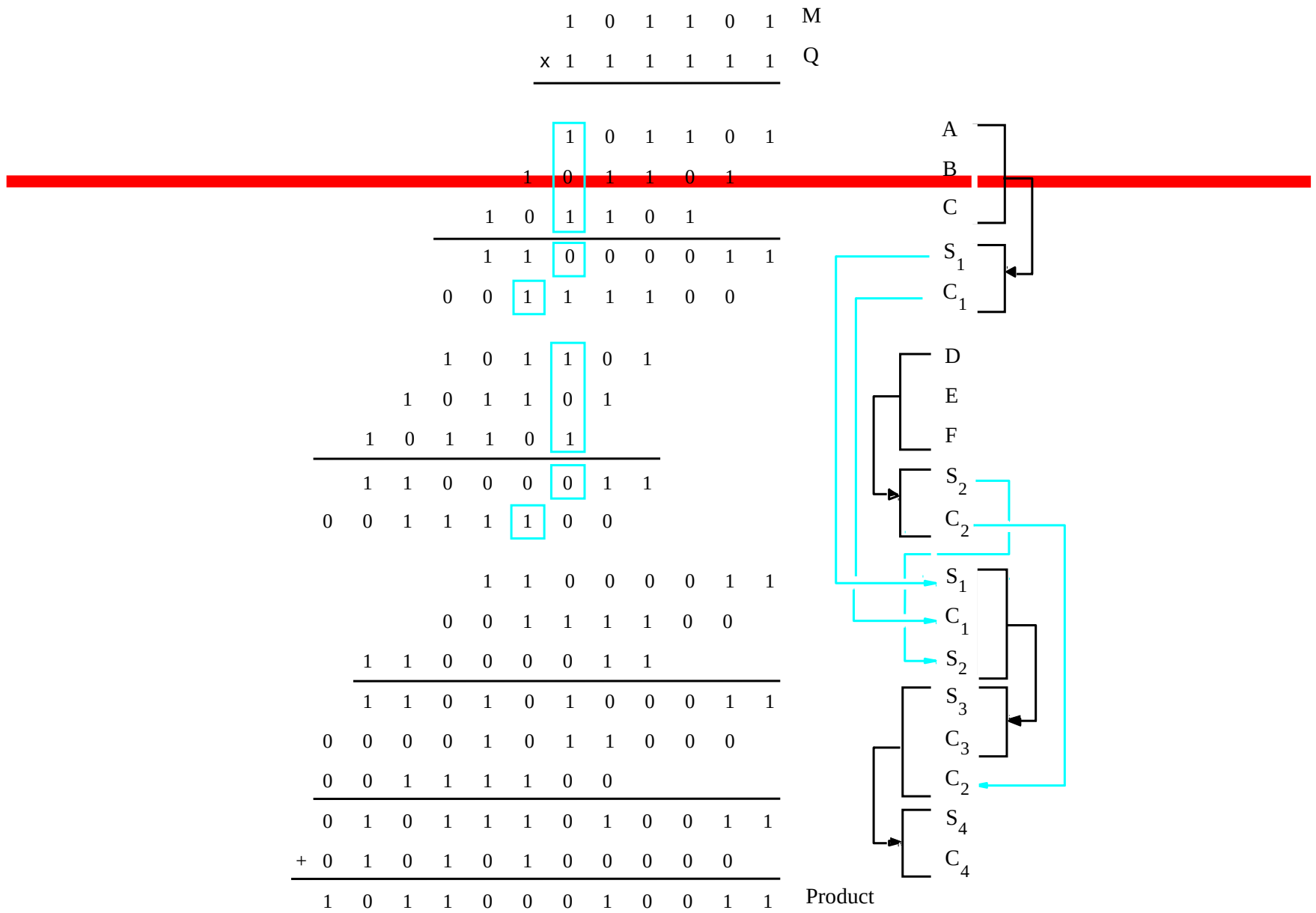


Figure 6.18. The multiplication example from Figure 6.17 performed using carry-save addition.

Integer Division

Manual Division

$$\begin{array}{r} 21 \\ 13 \overline{) 274} \\ \underline{26} \\ 14 \\ \underline{13} \\ 1 \end{array}$$

$$\begin{array}{r} 10101 \\ 1101 \overline{) 100010010} \\ \underline{1101} \\ 10000 \\ \underline{1101} \\ 1110 \\ \underline{1101} \\ 1 \end{array}$$

Longhand division examples.

Longhand Division Steps

- Position the divisor appropriately with respect to the dividend and performs a subtraction.
- If the remainder is zero or positive, a quotient bit of 1 is determined, the remainder is extended by another bit of the dividend, the divisor is repositioned, and another subtraction is performed.
- If the remainder is negative, a quotient bit of 0 is determined, the dividend is restored by adding back the divisor, and the divisor is repositioned for another subtraction.

~~Circuit Arrangement~~

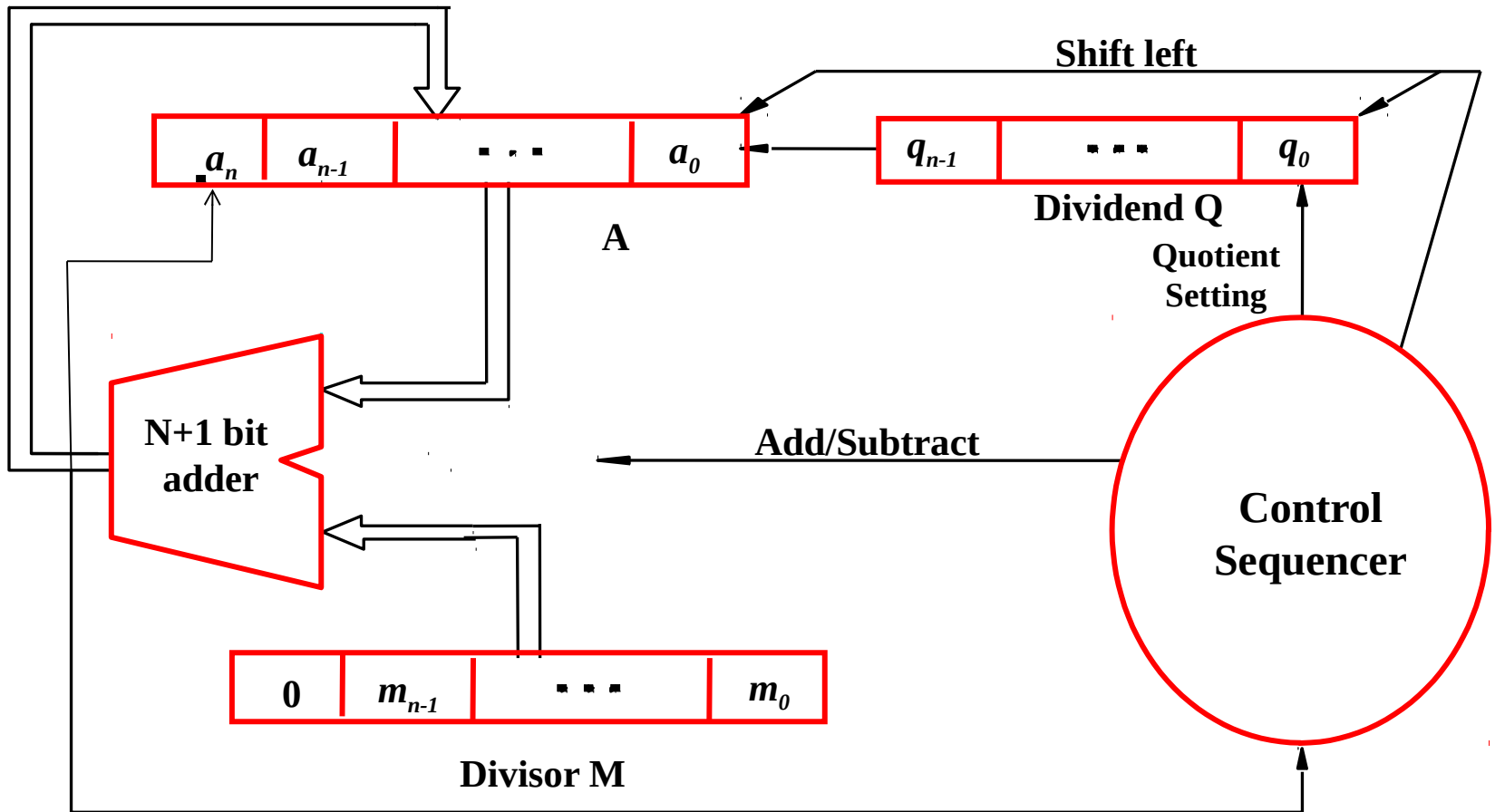


Figure 6.21. Circuit arrangement for binary division.

Restoring Division

- Shift A and Q left one binary position
- Subtract M from A, and place the answer back in A
- If the sign of A is 1, set q_0 to 0 and add M back to A (restore A); otherwise, set q_0 to 1
- Repeat these steps n times

Examples

$$\begin{array}{r}
 11 \overline{) 1000} \\
 \underline{11} \\
 10
 \end{array}$$


 


Figure 6.22. A restoring-division example.

Nonrestoring Division

- Avoid the need for restoring A after an unsuccessful subtraction.
- Any idea?
- Step 1: (Repeat n times)
 - If the sign of A is 0, shift A and Q left one bit position and subtract M from A; otherwise, shift A and Q left and add M to A.
 - Now, if the sign of A is 0, set q_0 to 1; otherwise, set q_0 to 0.
- Step2: If the sign of A is 1, add M to A

Examples

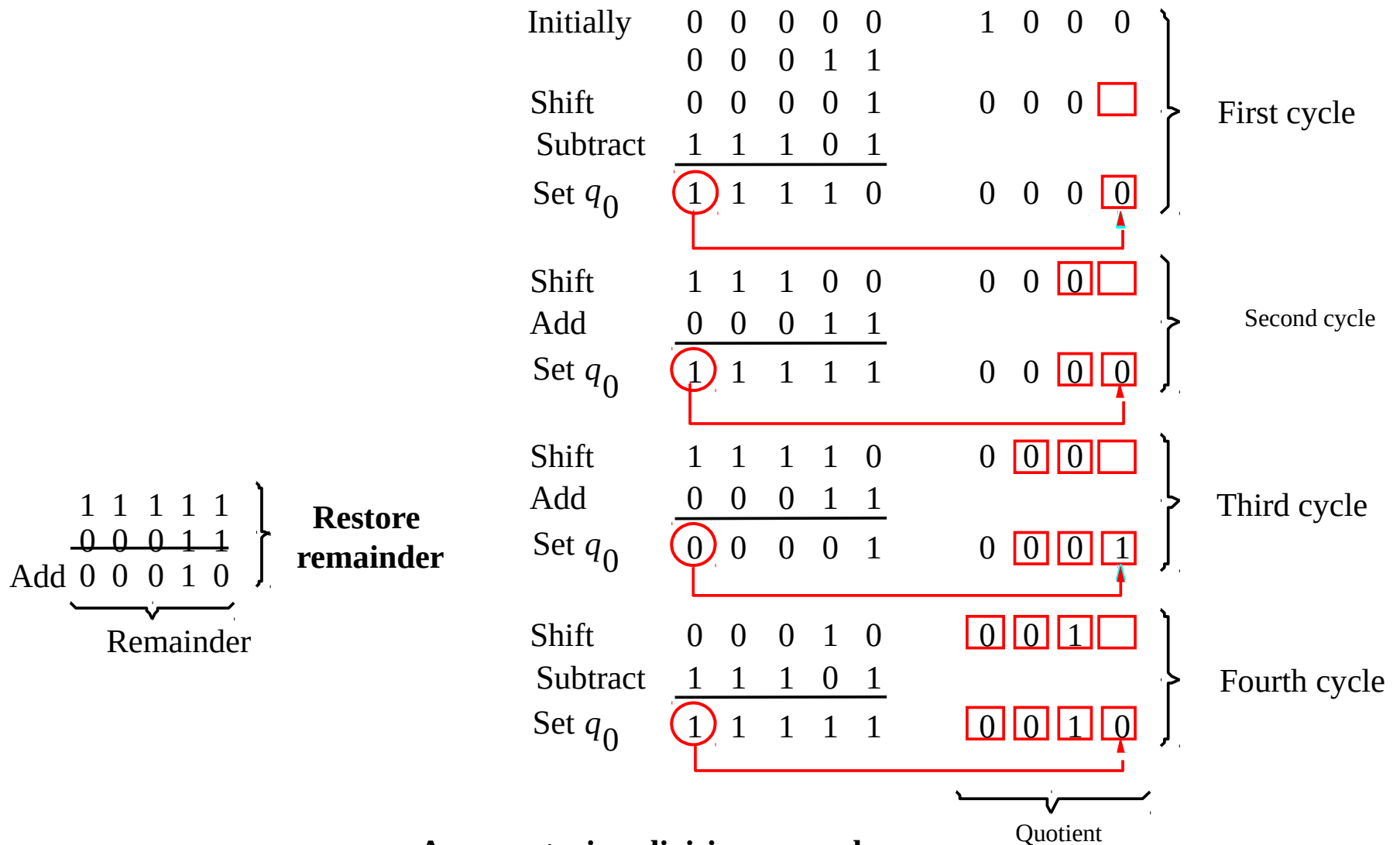


A nonrestoring-division example.

Division

- More complex than multiplication
- Negative numbers are really bad!
- Based on long division

Division of Unsigned Binary Integers

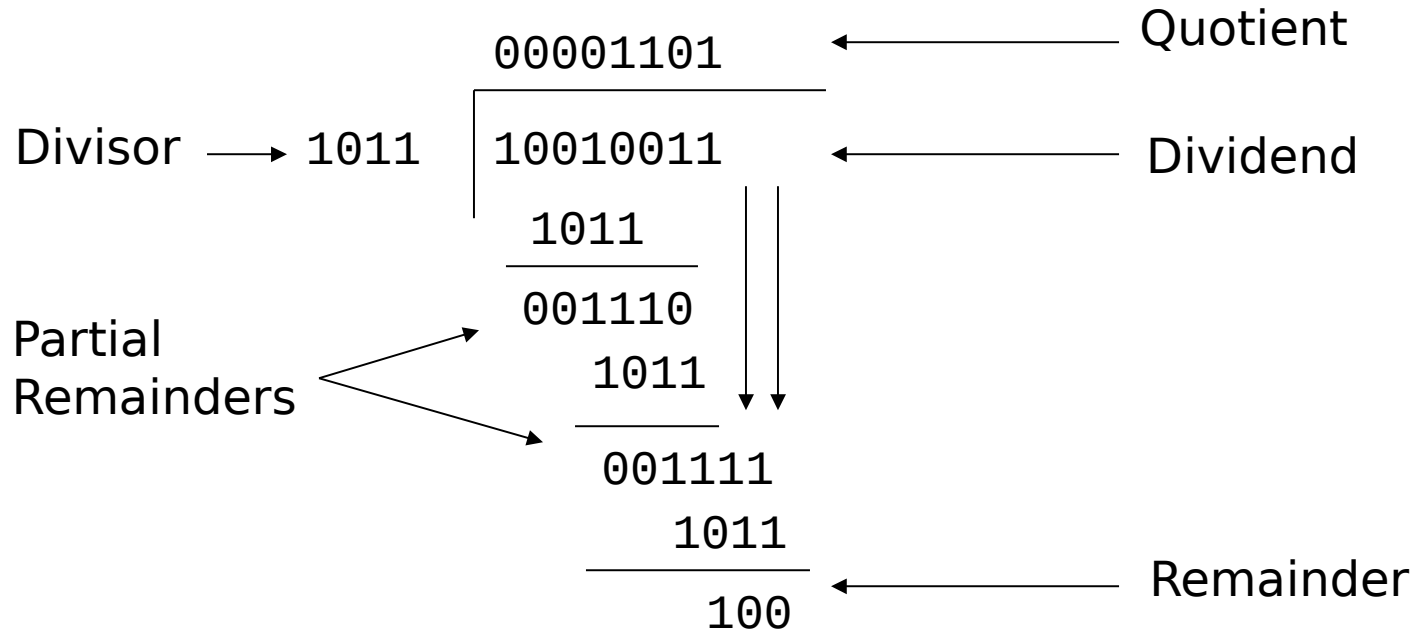

Flowchart for Unsigned Binary Division

